

Simplifying expressions

| Input | | | Output | |
|-------|---|-----------------|--------|------------------|
| A | B | C _{in} | S | C _{out} |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

- $C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$
- $C_{out} = BC_{in} + AC_{in} + AB$
- Simplification reduces complexity: faster, smaller circuit!

Karnaugh map

$$C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$$

| | | | |
|------------------|----|---|---|
| | | A | |
| | | 0 | 1 |
| BC _{in} | 00 | 0 | 0 |
| | 01 | 0 | 1 |
| | 11 | 1 | 1 |
| | 10 | 0 | 1 |

AC_{in} (purple dashed box around cells (01,1) and (11,1))

BC_{in} (orange dashed box around cells (11,0) and (11,1))

AB (blue dashed box around cells (10,1) and (11,1))

$$C_{out} = BC_{in} + AB + AC_{in}$$

A “tool” to help simplify boolean expressions
Like a “slide rule”: Useful but limited

A table listing “minterms”
Minterms written in Gray code order
One var value changes betw. col/row

Build from the initial boolean expr.
Put a “1” where a minterm is true

E.g., $AB'C_{in}$ has a 1

Now, to simplify:
Look for adjacent max rectangular groups with power of 2 elements, with at least one unique variable.
In such a group, some var is {0,1}
Eliminate that variable

Here's another one!
Groups can be vertical too.
They can even “wrap around”
Diagonals aren't allowed

- $C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$
- $S = A'B'C_{in} + A'BC_{in}' + AB'C_{in}' + ABC_{in}$

| | | A | |
|------------------|----|---|---|
| | | 0 | 1 |
| BC _{in} | 00 | 0 | 0 |
| | 01 | 0 | 1 |
| | 11 | 1 | 1 |
| | 10 | 0 | 1 |

AC_{in} (purple dashed box around cells (01,1) and (11,1))
 BC_{in} (orange dashed box around cells (11,0) and (11,1))
 AB (blue dashed box around cells (11,1) and (10,1))

$$C_{out} = BC_{in} + AB + AC_{in}$$

| | | A | |
|------------------|----|---|---|
| | | 0 | 1 |
| BC _{in} | 00 | 0 | 1 |
| | 01 | 1 | 0 |
| | 11 | 0 | 1 |
| | 10 | 1 | 0 |

(Red dashed boxes around cells (00,1), (01,0), (11,1), and (10,0))

$$S = A'B'C_{in} + A'BC_{in}' + AB'C_{in}' + ABC_{in}$$

Four (or more?) Variables

| | | CD | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| AB | 00 | 0 | 0 | 0 | 0 |
| | 01 | 0 | 0 | 0 | 0 |
| | 11 | 0 | 1 | 1 | 0 |
| | 10 | 0 | 1 | 1 | 0 |

Can you minimize this one?

In AB: B is both {0,1}

In CD: C is both {0,1}

Eliminate B, C

Thus, we have just AD

| | | CD | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| AB | 00 | 0 | 0 | 0 | 0 |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | 1 | 1 | 1 | 1 |
| | 10 | 0 | 0 | 0 | 0 |

Can you minimize this one?

C,D both have {0,1}

A has {0,1}

Eliminate A,C,D

Thus, we have just B

Four (or more?) Variables

| | | CD | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| AB | 00 | 1 | 0 | 0 | 1 |
| | 01 | 0 | 0 | 0 | 0 |
| | 11 | 0 | 0 | 0 | 0 |
| | 10 | 1 | 0 | 0 | 1 |

Can you minimize this one?

Combine on top row

Combine on bottom row

$A'B'D'$

$AB'D'$


These terms can now combine

Thus, we have $B'D'$

Karnaugh Maps (K-Maps) are a simple calculation tool.

In practice, sophisticated logic synthesis algorithms/tools are used.

Multiplexor (aka MUX)

 


$S=0$
 $Y = (S) \quad ? B:A;$


when $S =$
 0: output A
 1: output B

| S | A | B | Y |
|---|---|---|---|
| 0 | 0 | x | 0 |
| 0 | 1 | x | 1 |
| 1 | x | 0 | 0 |
| 1 | x | 1 | 1 |


$$Y = S'A + SB$$

 

A 32-bit MUX

 

a. A 32-bit wide 2-to-1 multiplexor

 


b. The 32-bit wide multiplexor is actually an array of 32 1-bit multiplexors

Use 32 1-bit muxes
Each mux selects 1 bit


The same 1-bit Select (S) is
connected to each mux

Building a 1-bit ALU

 - ALU = arithmetic logic unit = arithmetic unit + logic unit



 1 Let's start small: Choose (select) betw. AND and OR




2 Now, introduce addition to ALU

Building a 32-bit ALU


**Can you build a 2-bit
ALU that does +, AND, OR?**

Let's try it!

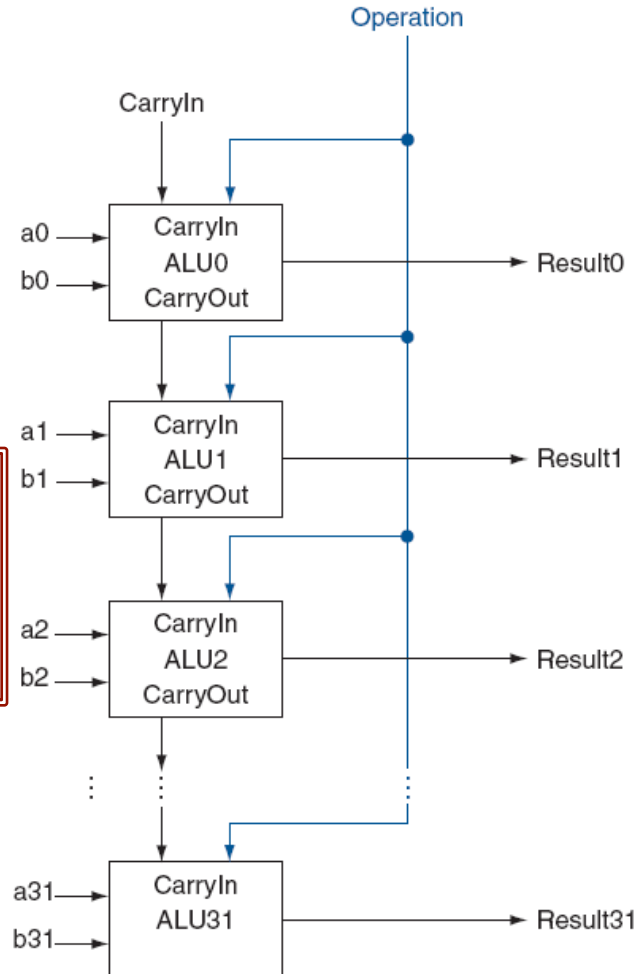

Implementing “sub”

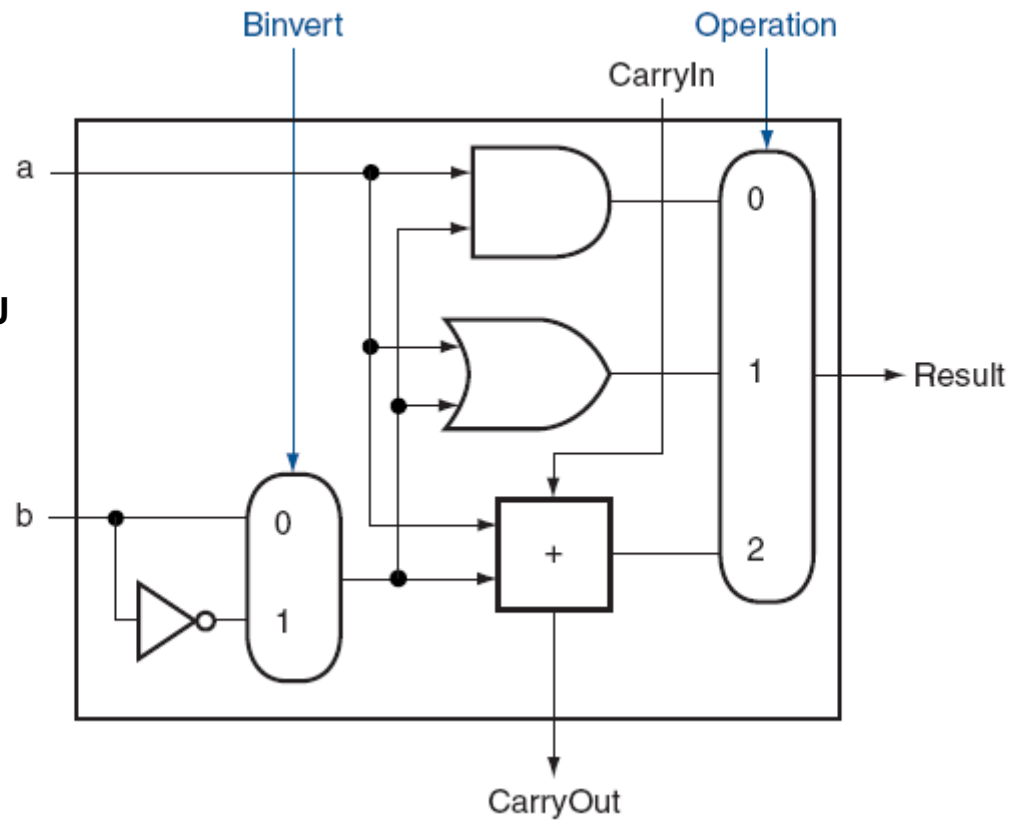Binvert=1
CarryIn=1 for 1st 1-bit ALU
Operation=2




Implementing NAND and NOR


NOR:
NOT (A OR B)
by DeMorgan's Law:
(NOT A) AND (NOT B)

Thus,
Operation=0,
Ainvert=1,
Binvert=1


And, NAND???

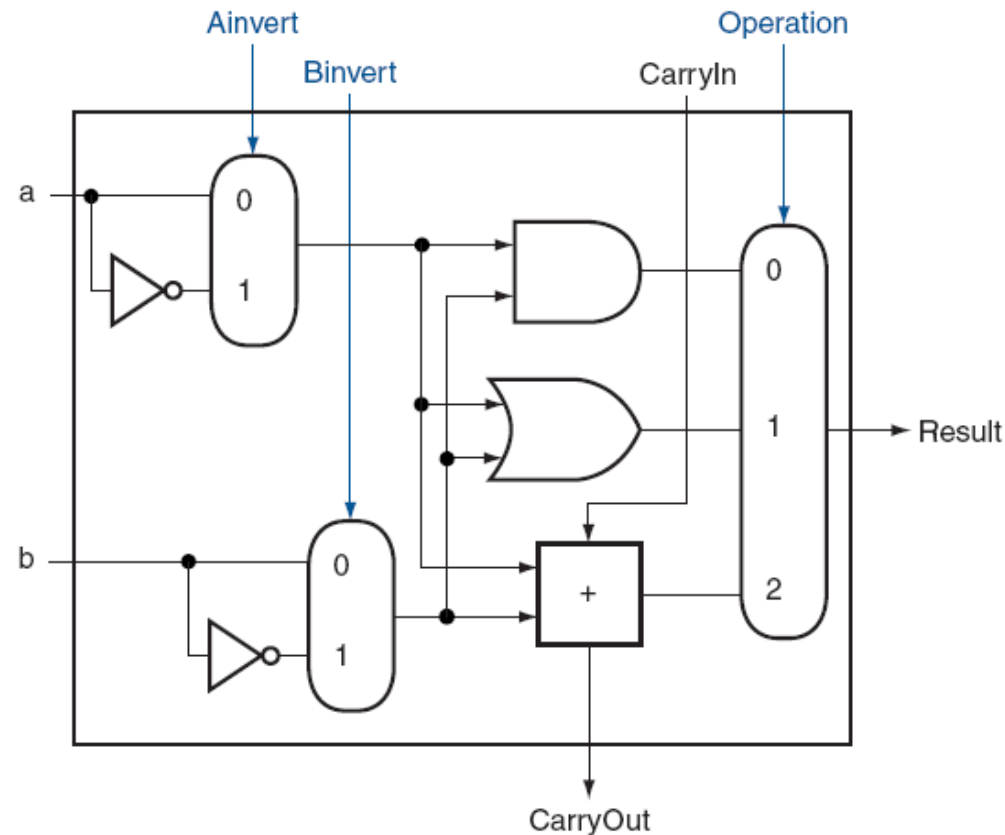

Implementing SLT (set-less-than)

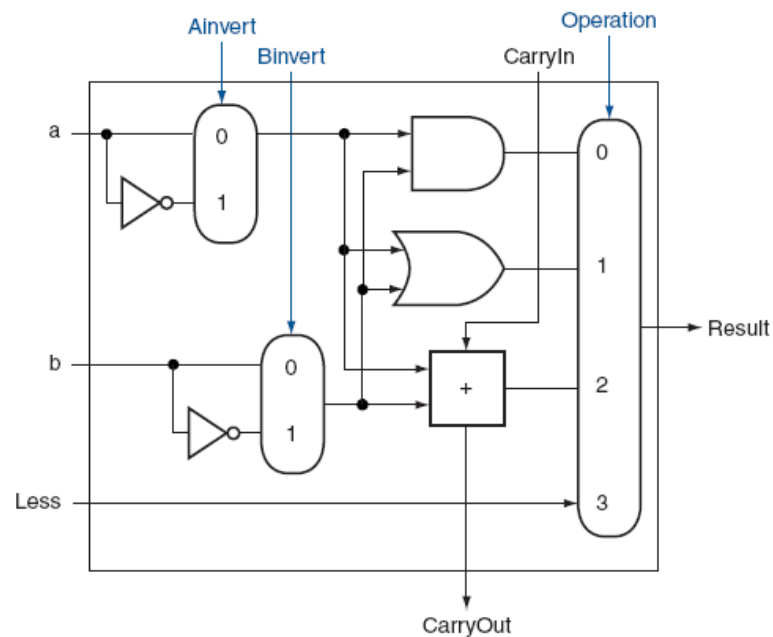

1-bit ALU for bits 0~30

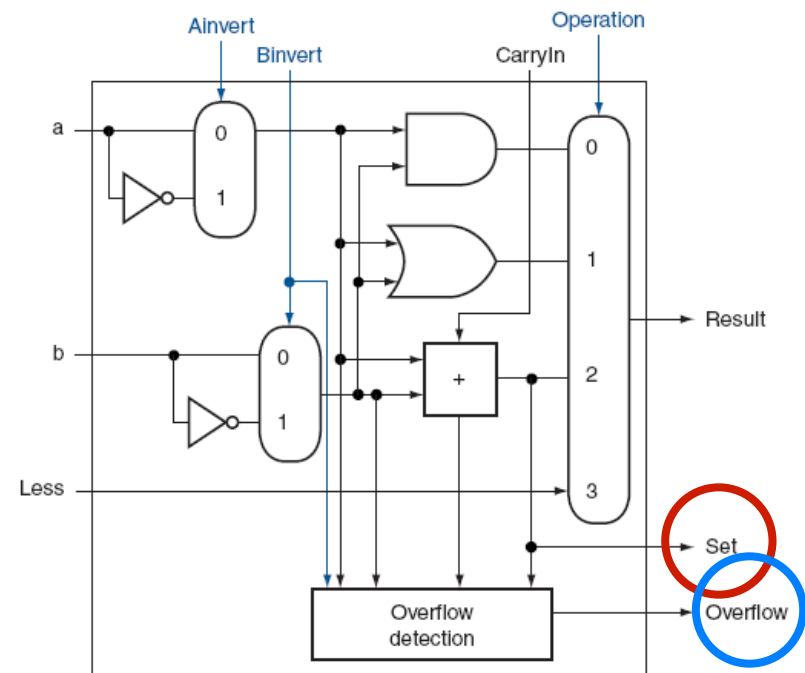

1-bit ALU for bit 31

Supporting BEQ and BNE

BEQ uses subtraction

beq \$t0,\$t1,LABEL
perform \$t0-\$t1
result=0 → equality

Setting the control

subtract (Cin=1,Binvert=1)
select result (operation=2)
detect zero result

