 


Multiplexor (aka MUX)


An example, yet VERY useful circuit!



when $S =$
0: output A
1: output B

S	A	B	Y
0	0	x	0
0	1	x	1
1	x	0	0
1	x	1	1

$$Y = S'A + SB$$

 

Simplifying expressions

Input			Output	
A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- $C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$
- $C_{out} = BC_{in} + AC_{in} + AB$
- Simplification reduces complexity: faster, smaller circuit!

Karnaugh map

$$C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$$

		A	
		0	1
BC _{in}	00	0	0
	01	0	1
	11	1	1
	10	0	1

$$C_{out} = BC_{in} + AB + AC_{in}$$

A "tool" to help simplify boolean expressions
Like a "slide rule": Useful but limited

A table listing "minterms"
Minterms written in Gray code order
One var value changes betw. col/row

Build from the initial boolean expr.
Put a "1" where a minterm is true
E.g., $AB'C_{in}$ has a 1

Now, to simplify:
Look for adjacent max rectangular groups with power of 2 elements.
In such a group, some var is {0,1}
Eliminate that variable

Here's another one!
Groups can be vertical too.
They can even "wrap around"
They can also overlap
Diagonals aren't allowed

- $C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$
- $S = A'B'C_{in} + A'BC_{in}' + AB'C_{in}' + ABC_{in}$

		A	
		0	1
BC _{in}	00	0	0
	01	0	1
	11	1	1
	10	0	1

$$C_{out} = BC_{in} + AB + AC_{in}$$

		A	
		0	1
BC _{in}	00	0	1
	01	1	0
	11	0	1
	10	1	0

$$S = A'B'C_{in} + A'BC_{in}' + AB'C_{in}' + ABC_{in}$$

Four (or more?) Variables

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	0	0	0	0
	11	0	1	1	0
	10	0	1	1	0

Can you minimize this one?

In AB: B is both {0,1}
In CD: C is both {0,1}

Eliminate B, C
Thus, we have just AD

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

Can you minimize this one?

C,D both have {0,1}
A has {0,1}

Eliminate A,C,D
Thus, we have just B

CS/CoE1541: Intro. to Computer Architecture

University of Pittsburgh

32

Four (or more?) Variables

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	0	0	1

Can you minimize this one?

Combine on top row
Combine on bottom row

$A'B'D'$
 $AB'D'$

These terms can now combine
Thus, we have $B'D'$

Karnaugh Maps (K-Maps) are a simple calculation tool.

In practice, sophisticated logic synthesis algorithms/tools are used.


CS/CoE1541: Intro. to Computer Architecture

University of Pittsburgh

33

In-class Example

 - A device called a “7 segment LED digit”
- There are 8 LEDs – one for seven “segments” of a numeral and 1 for a decimal point




- **Problem**

- Given a 3-bit number, draw the corresponding numeral
- E.g., 000 is the numeral 0, 001 is numeral 1 and so forth

- **Solution**

- Create a Boolean function for each segment. Ignore the decimal point.
- Boolean function over three inputs for the 3-bit number.

- **Let's try it!!**

 

Segments numbered d0 to d7



Hex Digit LED



7 segments, 1 decimal point



Turn each segment on/off



State: 0=OFF, 1=ON

“Draw” numbers 0 to 9

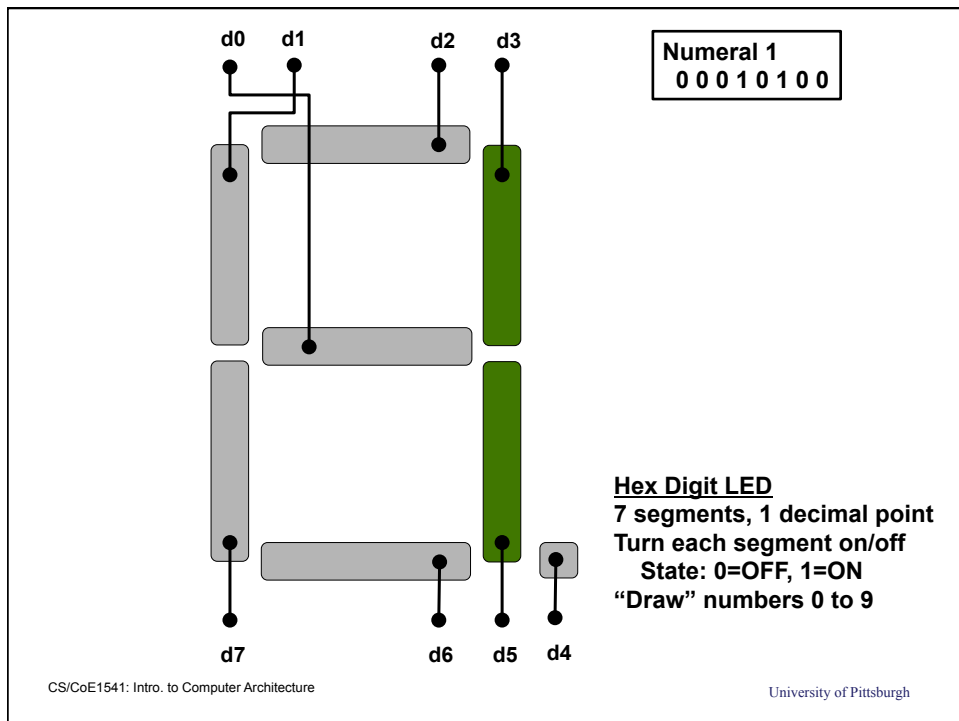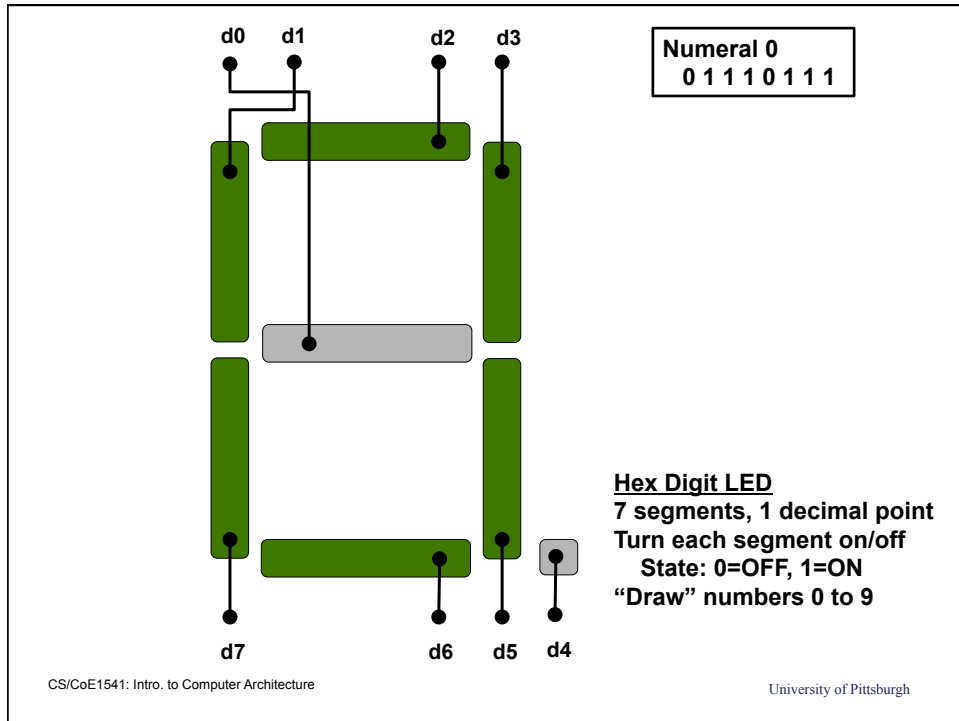

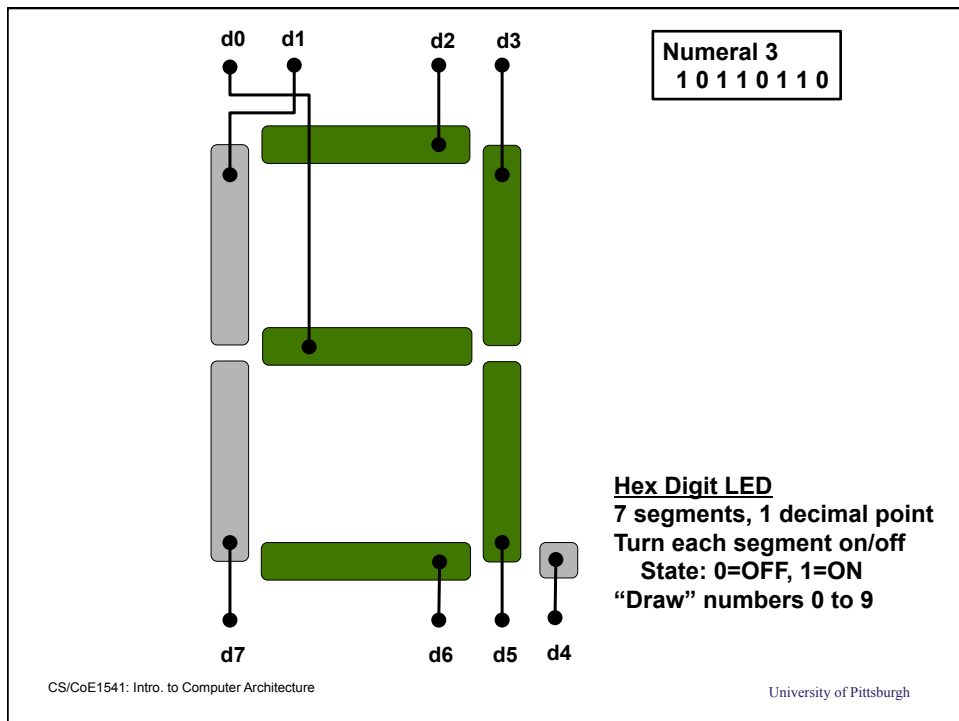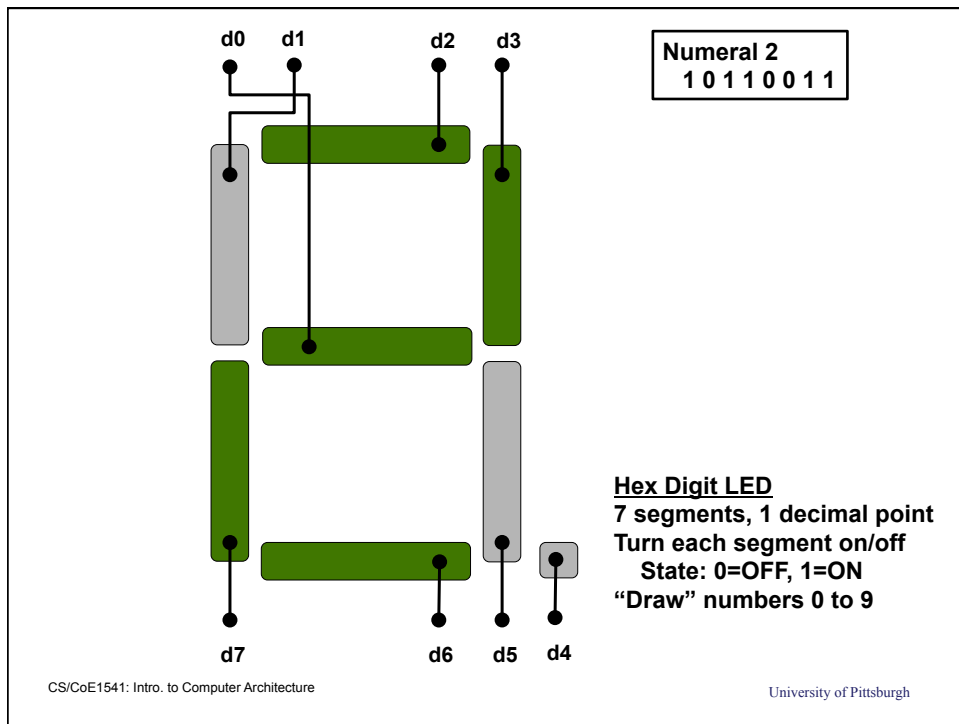

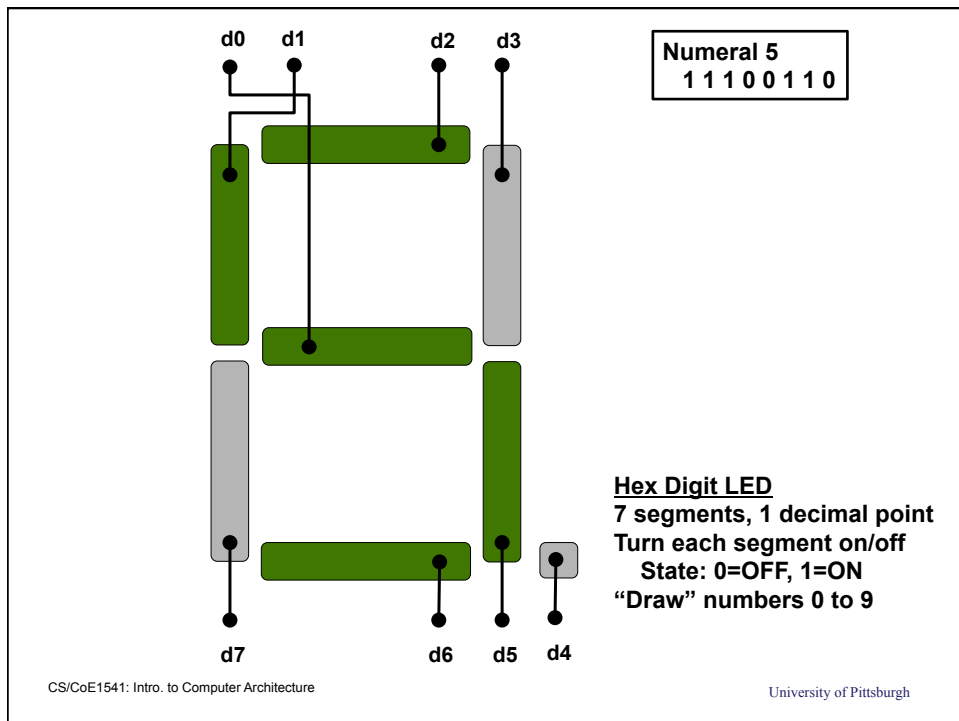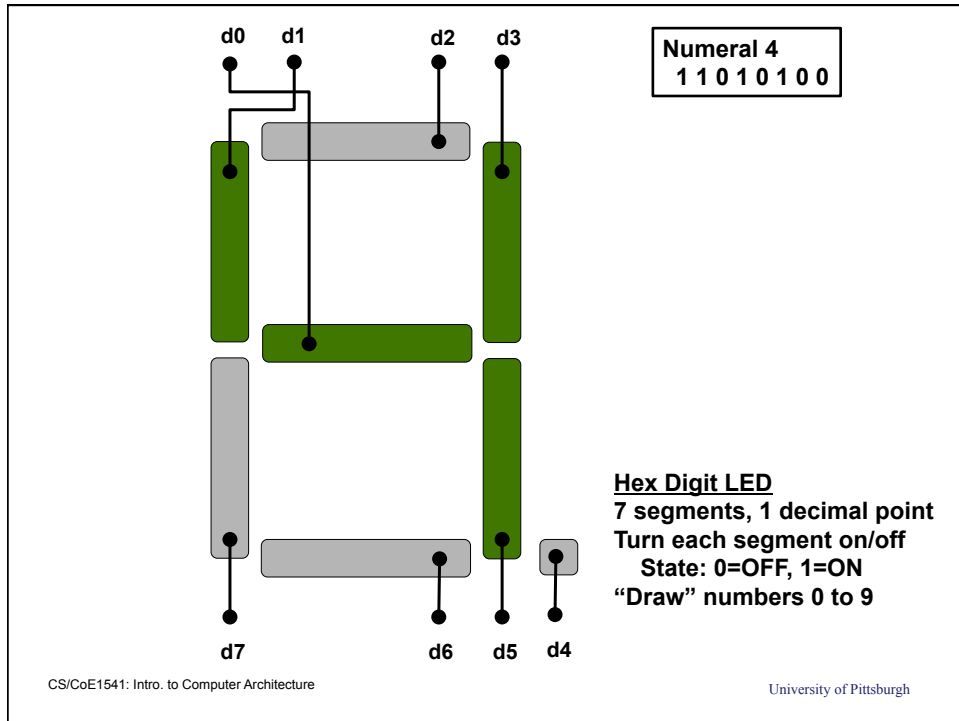

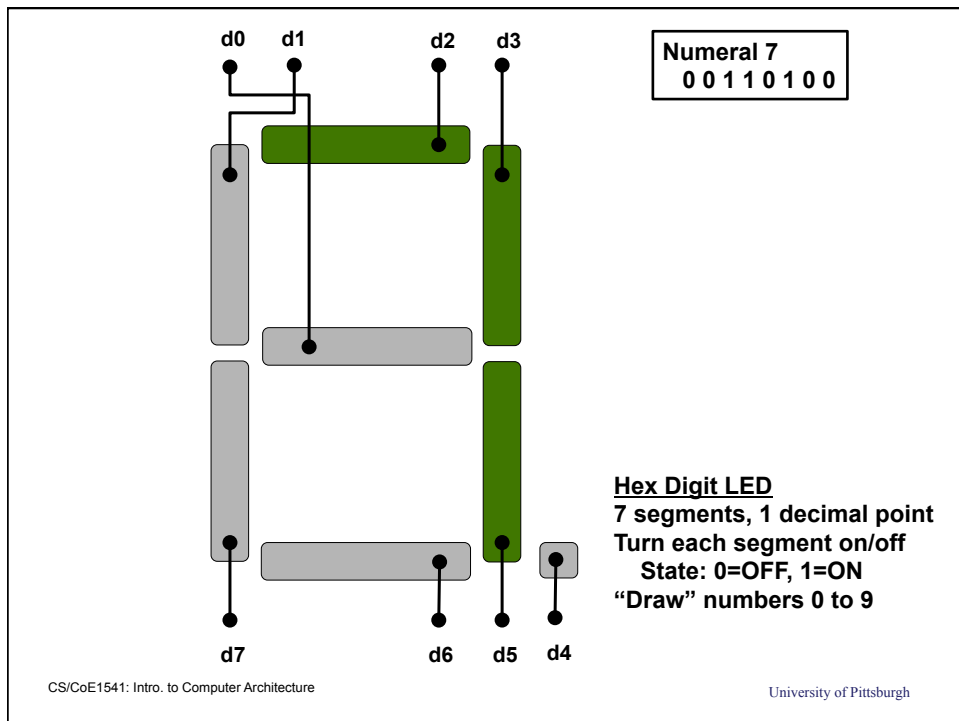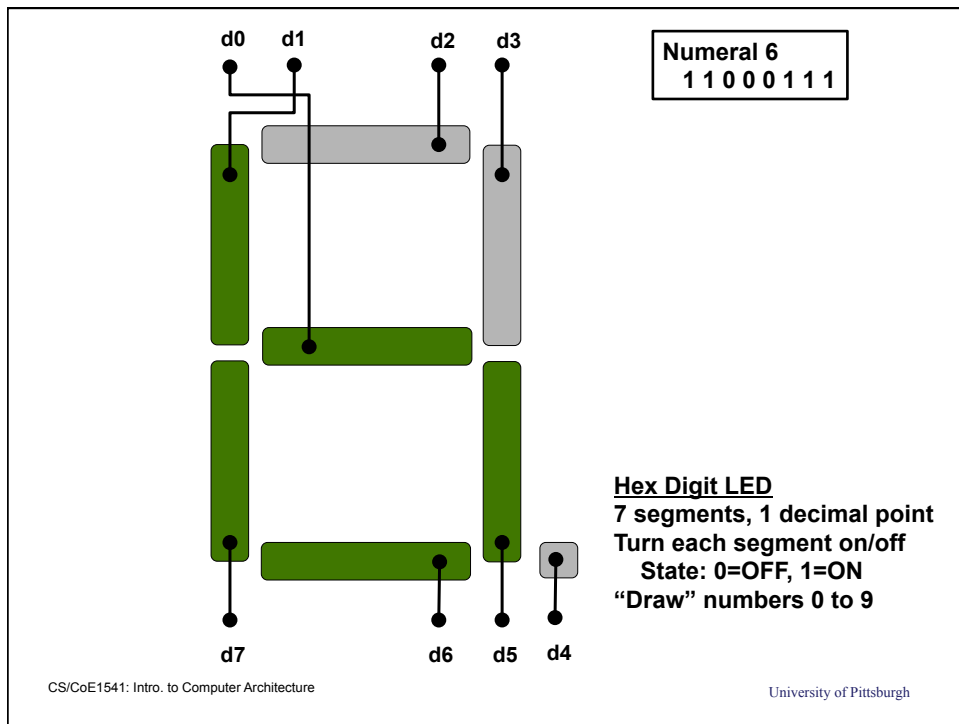

In-class Example

- Create a truth table
- Inputs are numbered i0 to i2 (3 bits)
- Outputs are numbered d0 to d7, corresponding to segments
- “Draw” the numerals by setting d0 to d7 to 1s or 0s.

inputs			outputs							
i2	i1	i0	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

Input: 3-bit number

Outputs: Segments for the LED hex digit

inputs			outputs							
i2	i1	i0	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	1	1	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	0	1	1
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

Fill in the truth table for each numeral
 Numerals 0 to 2 are shown.
 Can you complete 3 to 7?

inputs			outputs							
i2	i1	i0	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	1	1	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	0	1	1
0	1	1	1	0	1	1	0	1	1	0
1	0	0	1	1	0	1	0	1	0	0
1	0	1	1	1	1	0	0	1	1	0
1	1	0	1	1	0	0	0	1	1	1
1	1	1	0	0	1	1	0	1	0	0

Completed truth table
 Now, write down the *minimal* (simplified) Boolean functions
 Use a K-map to minimize each one!

inputs			outputs							
i2	i1	i0	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	1	1	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	0	1	1
0	1	1	1	0	1	1	0	1	1	0
1	0	0	1	1	0	1	0	1	0	0
1	0	1	1	1	1	0	0	1	1	0
1	1	0	1	1	0	0	0	1	1	1
1	1	1	0	0	1	1	0	1	0	0

Completed truth table

Now, write down the *minimal* (simplified) Boolean functions

Use a K-map to minimize each one!

		i1, i0			
		00	01	11	10
i2	0				
	1				

Use a K-map for each output function – d0 to d7

Let's start with d0

We'll only do a few – d0, d3 and d5

Can you do the rest on your own???

Function d0

i1, i0

		00	01	11	10
i2	0	0	0	1	1
	1	1	1	0	1

i2	i1	i0	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	1	1	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	0	1	1
0	1	1	1	0	1	1	0	1	1	0
1	0	0	1	1	0	1	0	1	0	0
1	0	1	1	1	1	0	0	1	1	0
1	1	0	1	1	0	0	0	1	1	1
1	1	1	0	0	1	1	0	1	0	0

Function d0

i1, i0

		00	01	11	10
i2	0	0	0	1	1
	1	1	1	0	1

i2	i1	i0	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	1	1	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	0	1	1
0	1	1	1	0	1	1	0	1	1	0
1	0	0	1	1	0	1	0	1	0	0
1	0	1	1	1	1	0	0	1	1	0
1	1	0	1	1	0	0	0	1	1	1
1	1	1	0	0	1	1	0	1	0	0

3 terms
i2'i1
i2i1'
i2i0

$$d0 = \overline{i2}i1 + i2\overline{i1} + i2i0$$

Function d3

i1, i0

		00	01	11	10
i2	0	1	1	1	1
	1	1	0	1	0

i2	i1	i0	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	1	1	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	0	1	1
0	1	1	1	0	1	1	0	1	1	0
1	0	0	1	1	0	1	0	1	0	0
1	0	1	1	1	1	0	0	1	1	0
1	1	0	1	1	0	0	0	1	1	1
1	1	1	0	0	1	1	0	1	0	0

Function d3

i1, i0

		00	01	11	10
i2	0	1	1	1	1
	1	1	0	1	0

i2	i1	i0	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	1	1	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	0	1	1
0	1	1	1	0	1	1	0	1	1	0
1	0	0	1	1	0	1	0	1	0	0
1	0	1	1	1	1	0	0	1	1	0
1	1	0	1	1	0	0	0	1	1	1
1	1	1	0	0	1	1	0	1	0	0

$$d3 = \overline{i2} + \overline{i1}i0 + i1i0$$

Function d5

i1, i0

		00	01	11	10
i2	0	1	1	1	0
	1	1	1	1	1

i2	i1	i0	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	1	1	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	0	1	1
0	1	1	1	0	1	1	0	1	1	0
1	0	0	1	1	0	1	0	1	0	0
1	0	1	1	1	1	0	0	1	1	0
1	1	0	1	1	0	0	0	1	1	1
1	1	1	0	0	1	1	0	1	0	0

Function d5


i1, i0

		00	01	11	10
i2	0	1	1	1	0
	1	1	1	1	1

i2	i1	i0	d0	d1	d2	d3	d4	d5	d6	d7
0	0	0	0	1	1	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	0	1	1
0	1	1	1	0	1	1	0	1	1	0
1	0	0	1	1	0	1	0	1	0	0
1	0	1	1	1	1	0	0	1	1	0
1	1	0	1	1	0	0	0	1	1	1
1	1	1	0	0	1	1	0	1	0	0

$$d5 = \overline{i1} + i0 + i2$$

 
Completed Circuit with all functions d0 to d7



Outputs to the LED hex digit

See example: LEDhexdigit.circ

A 32-bit MUX

 


a. A 32-bit wide 2-to-1 multiplexer

 
b. The 32-bit wide multiplexer is actually an array of 32 1-bit multiplexers

Building a 1-bit ALU

- ALU = arithmetic logic unit = arithmetic unit + logic unit




Building a 32-bit ALU

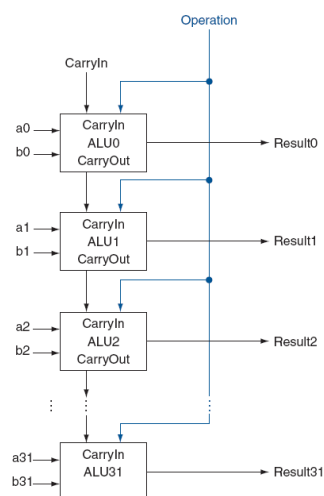

Implementing “sub”

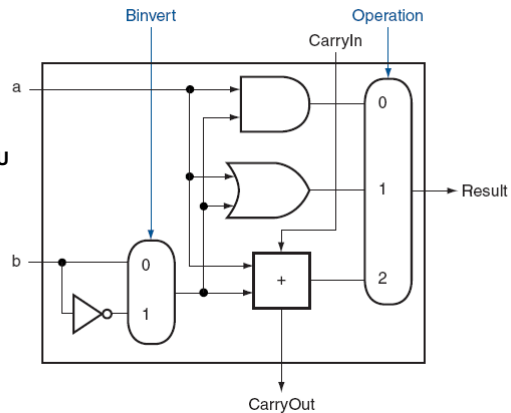Binvert=1
CarryIn=1 for 1st 1-bit ALU
Operation=2




Implementing NAND and NOR


NOR:
NOT (A OR B)
by DeMorgan's Law:
(NOT A) AND (NOT B)

Thus,
Operation=0,
Ainvert=1,
Binvert=1


And, NAND???

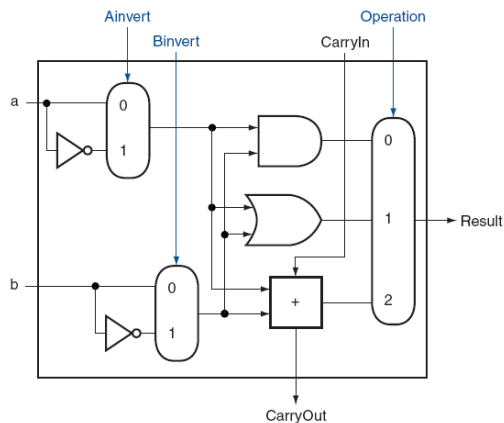

Implementing SLT (set-less-than)

 

1-bit ALU for bits 0~30

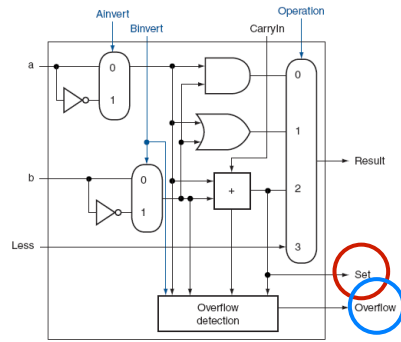

1-bit ALU for bit 31

Implementing SLT (set-less-than)

SLT uses subtraction

slt \$t0,\$t1,\$t2

\$t1 < \$t2: \$t1-\$t2 gives negative result
set is 1 when negative


Setting the control

perform subtraction (Cin=1, Binvert=1)

select Less as output (Operation=3)

ALU31's Set connected to ALU0 Less

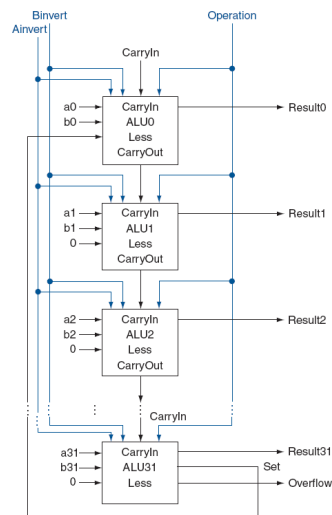Why do we need Set? Could we use just the Result31?




Supporting BEQ and BNE

BEQ uses subtraction


beq \$t0,\$t1,LABEL
perform \$t0-\$t1
result=0 → equality

Setting the control

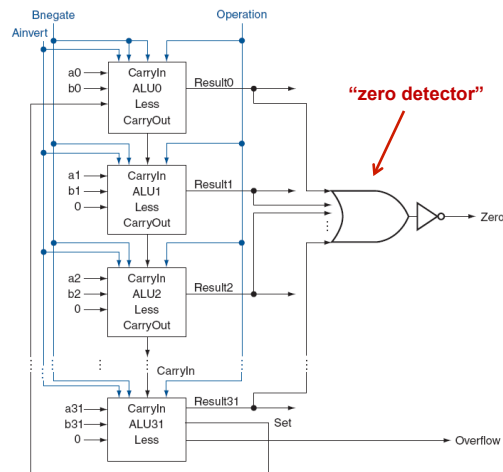subtract (Cin=1, Binvert=1)
select result (operation=2)
detect zero result



Abstracting ALU

 

- Note that ALU is a combinational logic