 


Multiplexor (aka MUX)

An example, yet **VERY** useful circuit!




$S=0$
 $Y = (S) ? B:A;$


when $S =$
 0 : output A
 1 : output B

S	A	B	Y
0	0	x	0
0	1	x	1
1	x	0	0
1	x	1	1


$$Y = S'A + SB$$

 

A 32-bit MUX

 

a. A 32-bit wide 2-to-1 multiplexor


 


b. The 32-bit wide multiplexor is actually an array of 32 1-bit multiplexors


Use 32 1-bit muxes
Each mux selects 1 bit
S is connected to each mux

Building a 1-bit ALU

  - ALU = arithmetic logic unit = arithmetic unit + logic unit




Building a 32-bit ALU

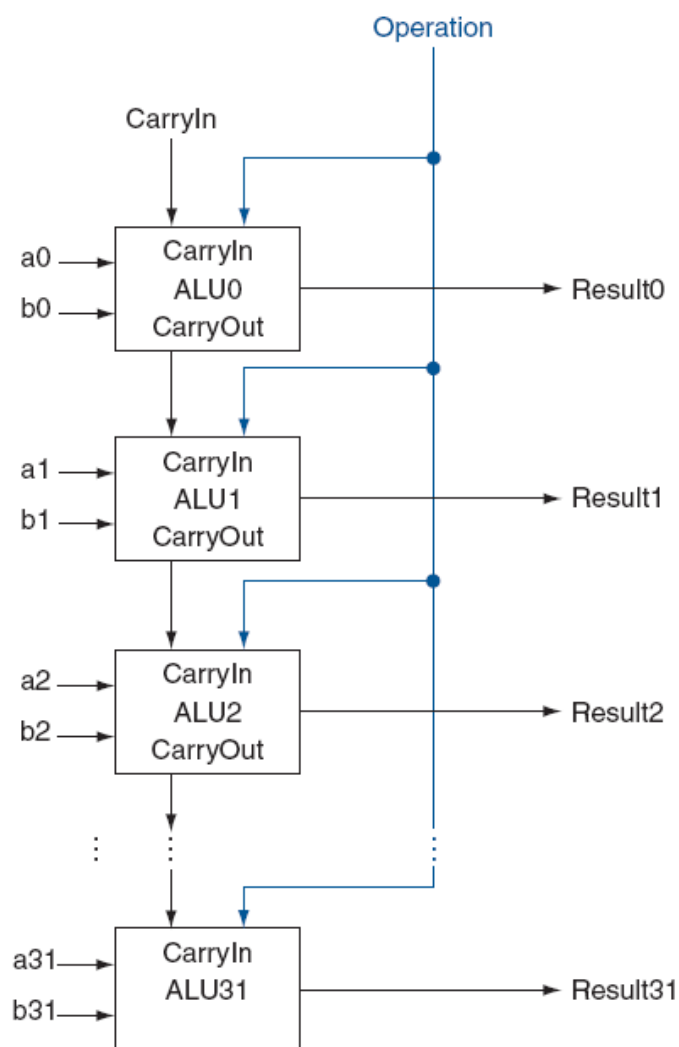

Implementing “sub”

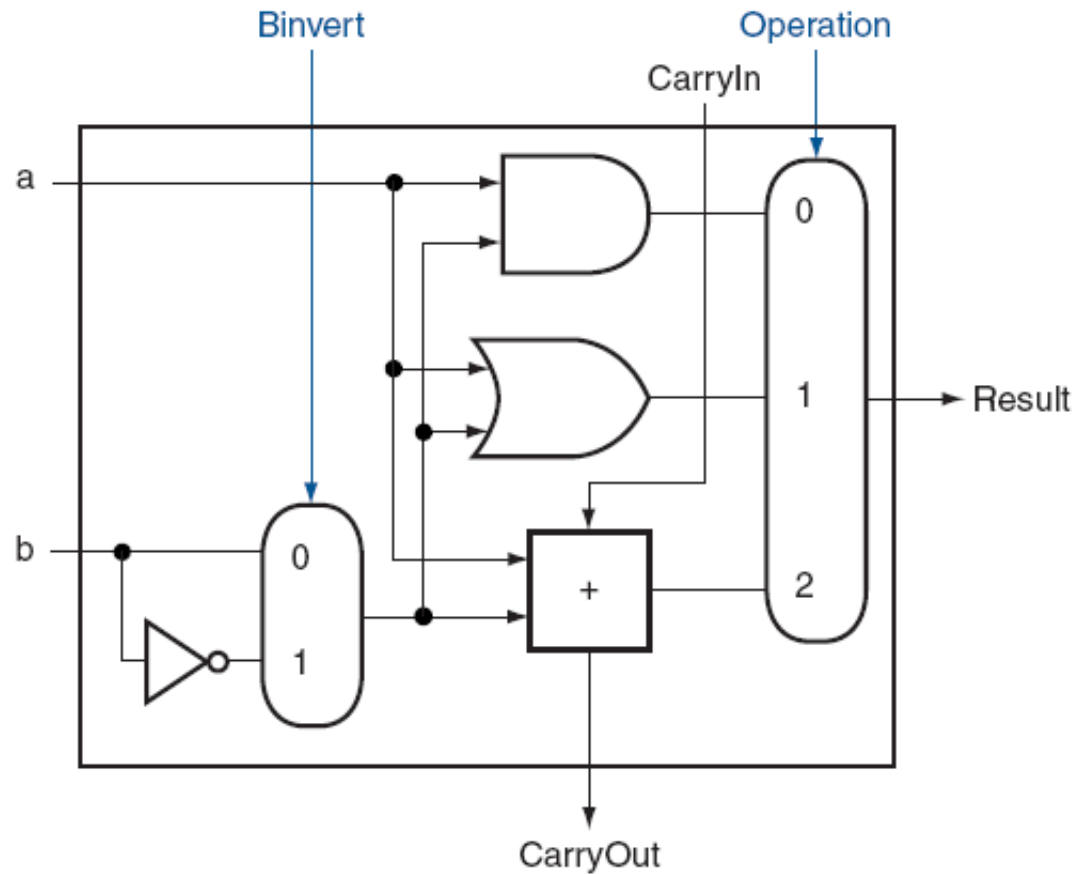Binvert=1
CarryIn=1 for 1st 1-bit ALU
Operation=2




Implementing NAND and NOR


NOR:
NOT (A OR B)
by DeMorgan's Law:
(NOT A) AND (NOT B)

Thus,
Operation=0,
Ainvert=1,
Binvert=1


And, NAND???

 

Implementing SLT (set-less-than)

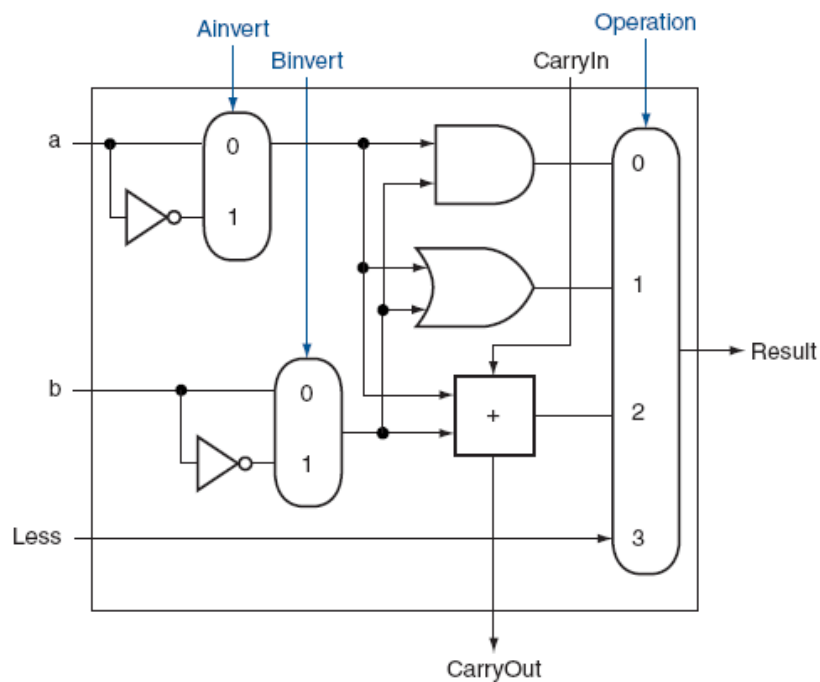

1-bit ALU for bits 0~30

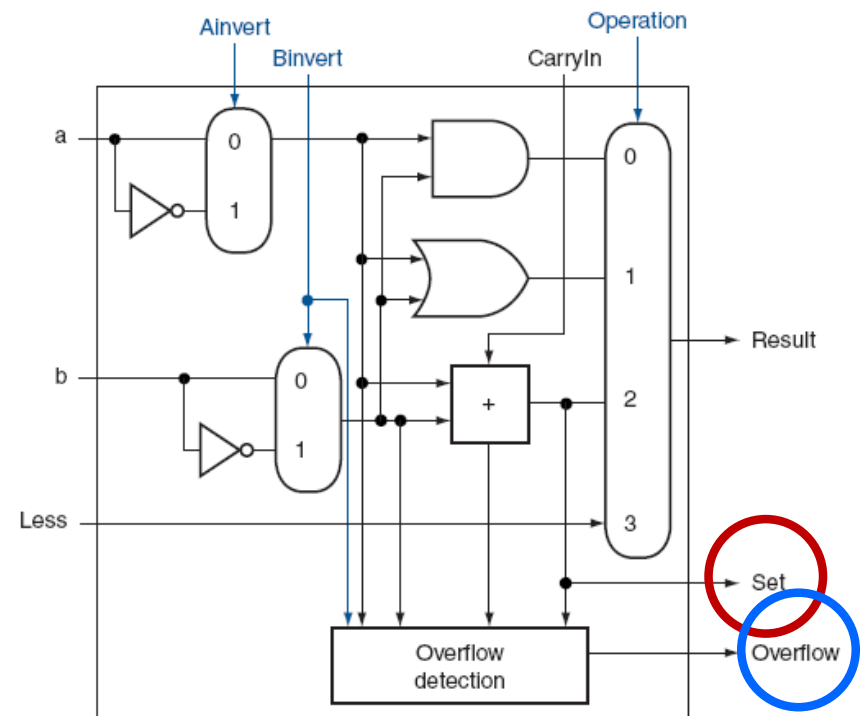

1-bit ALU for bit 31

Implementing SLT (set-less-than)

SLT uses subtraction


```
slt $t0,$t1,$t2
```

\$t1 < \$t2: \$t1-\$t2 gives negative result
set is 1 when negative

Setting the control

```
perform subtraction (Cin=1,Binvert=1)
select Less as output (Operation=3)
ALU31's Set connected to ALU0 Less
```

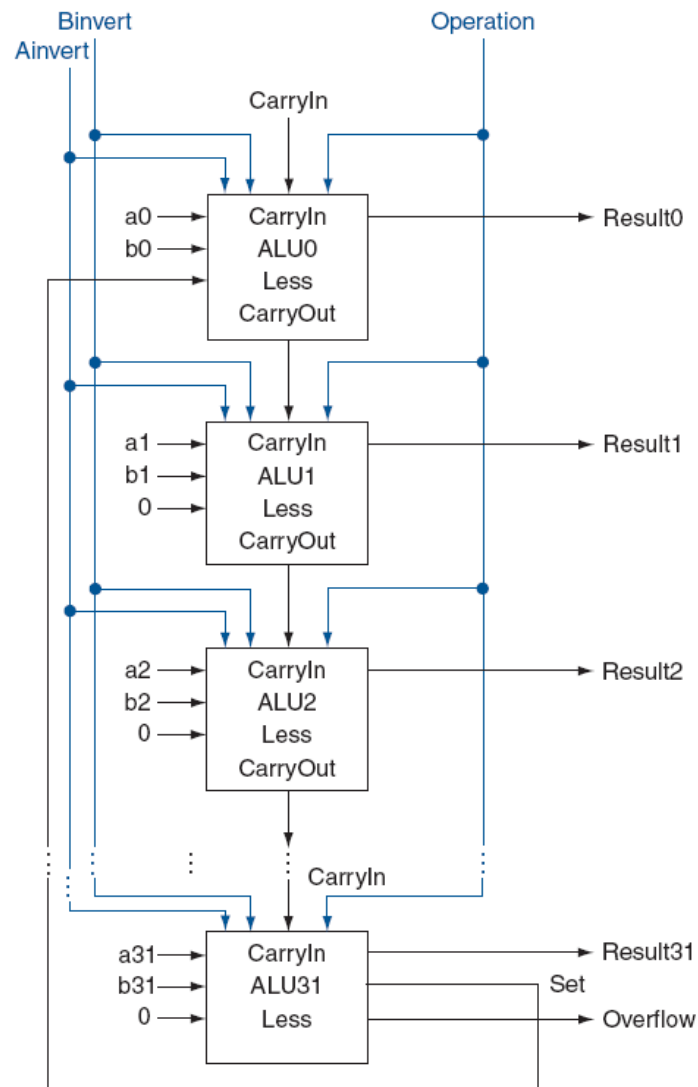Why do we need Set? Could we use just the Result31?




Supporting BEQ and BNE

BEQ uses subtraction


beq \$t0,\$t1,LABEL
perform \$t0-\$t1
result=0 → equality

Setting the control

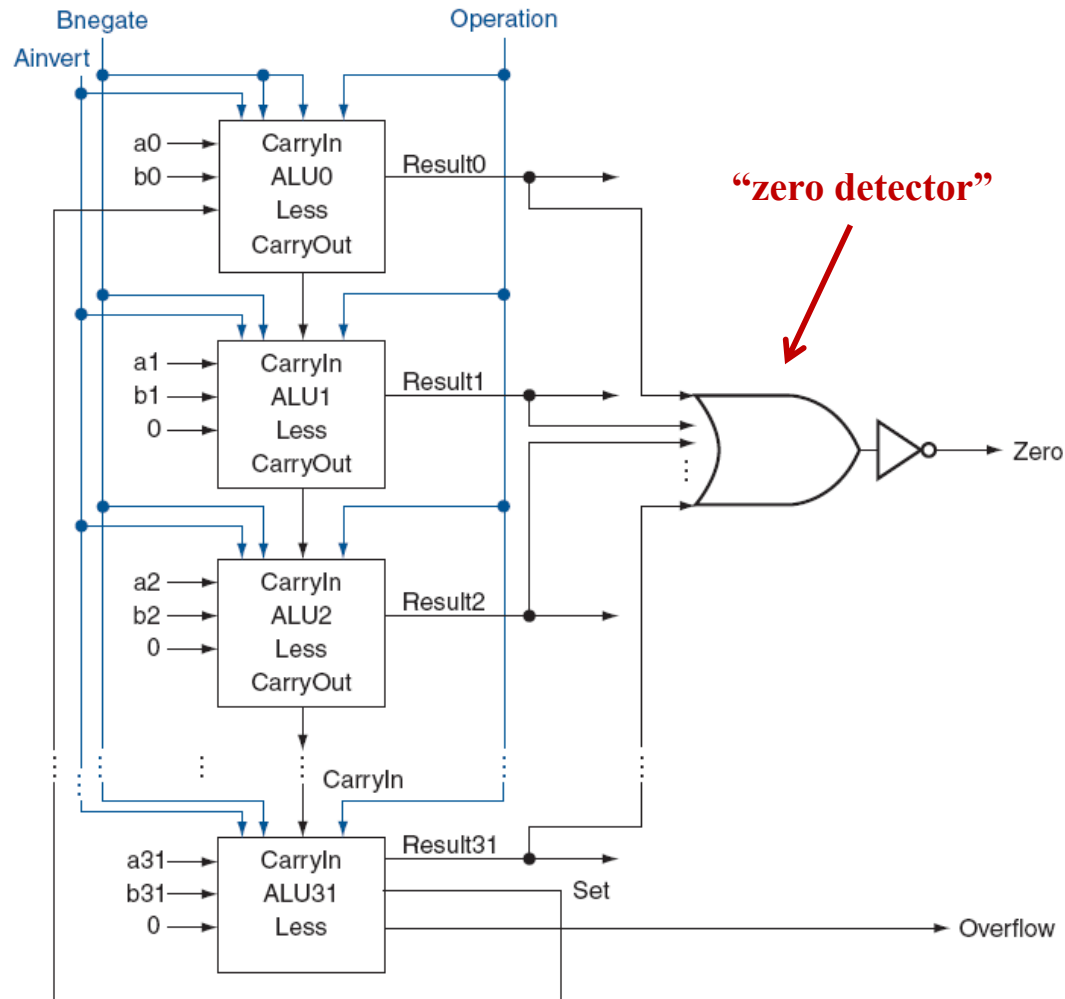subtract (Cin=1,Binvert=1)
select result (operation=2)
detect zero result



Abstracting ALU

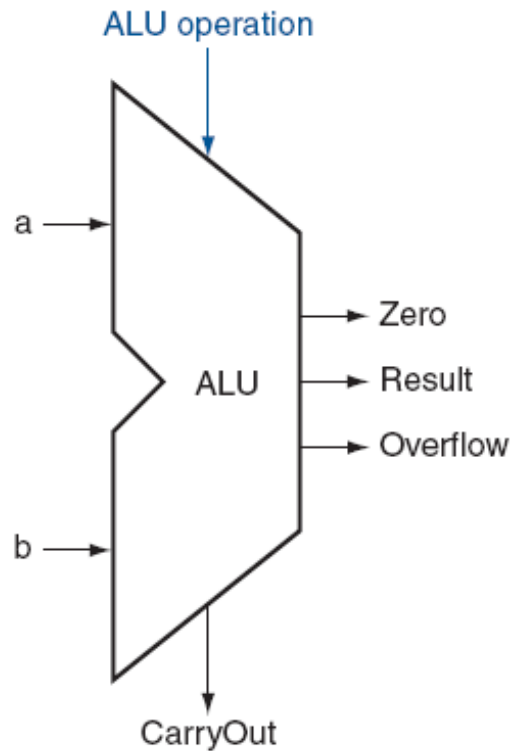


- Note that ALU is a combinational logic

Sequential Logic


- Output depends on *sequence of previous* inputs
 - “Sequence of previous inputs” – this is history
 - History is a state that captures how you get here
 - ♦ E.g., 25 cents vending = 10 cents + 10 cents + 5 cents
 - ♦ Or, 25 cents + 10 cents = 35 cents. Multiple ways are possible.
 - State requires memory – remembering the past...
- Memory in logic
 - Smallest element is 1 bit of memory
 - Use logic gates to create a 1-bit memory
 - Yet, combinational logic (using gates) depends on present inputs!
- Fundamental building block: “RS latch”
 - 1 bit of history through feedback of gates

RS latch

 


- Beware of the feedback!

RS latch

 


- When $R=0$, $S=1$

RS latch

 


- When $R=1$, $S=0$

RS latch

 


- When $R=0$, $S=0$, and Q was 0

RS latch

 

- When $R=0$, $S=0$, and Q was 1

RS latch

 

- What happens if $R=S=1$

RS latch truth table


R	S	Q(t)	Q(t+1)	
0	0	0	0	Storage (R=0, S=0)
0	0	1	1	
0	1	0	1	Set to 1 (S=1)
0	1	1	1	
1	0	0	0	Reset to 0 (R=0)
1	0	1	0	
1	1	0	Invalid	
1	1	1	Invalid	

Outputs will track any changes in the inputs!

R=1, S=1 must be avoid.


Desirable to control when to capture input state.

D latch

 


- Note that we have an RS latch in the back-end of this design

D latch

 

- Note that R, S inputs always get opposite values when $C=1$
- When $C=0$, $S=R=0 \Rightarrow$ RS latch remembers the previous value

D latch



 


“latched mode”


C	D	Q(t)
0	0	Q(t-1)
0	1	Q(t-1)
1	0	0
1	1	1

“transparent mode”

D latch

 
 
 


D flip-flop (D-FF)

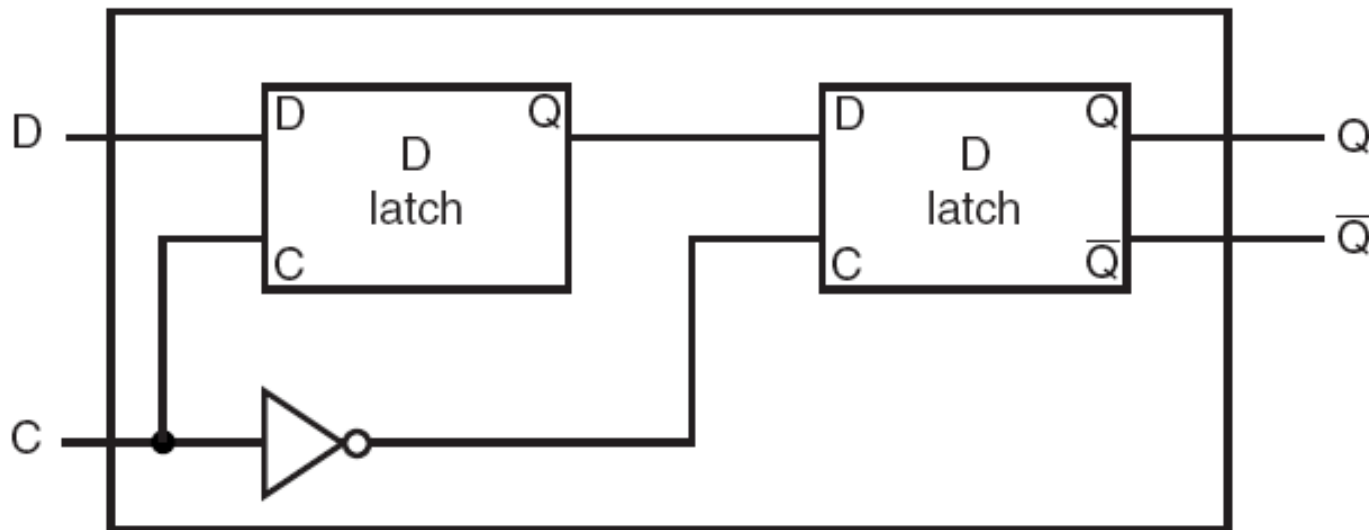


- Two cascaded D latches; C input of the second is inverted
- This is a negative edge (aka “falling edge”) triggered D-FF

D flip-flop

   

State Elements

 


RS latch

R,S control mode (reset, set, storage)

Q,Q' track R and S

R=1, S=1 invalid

 


D flip-flop (falling or negative edge triggered)

Two cascaded D latches

C=1 means 1st latch transparent, 2nd latched

C=0 means 1st latch latched, 2nd transparent

Output changes on falling edge (C: 1=>0)

 


D latch

C controls mode (0=latched, 1=transparent)

D is data input ("copied" during transparent)

Signal value triggered: Q,Q' track D when C=1

Guarantees R=1,S=1 can not be done

 


D flip-flop (rising or positive edge triggered)


Same as falling edge triggered

Output changes on rising edge (C: 0=>1)

Signaling Behavior

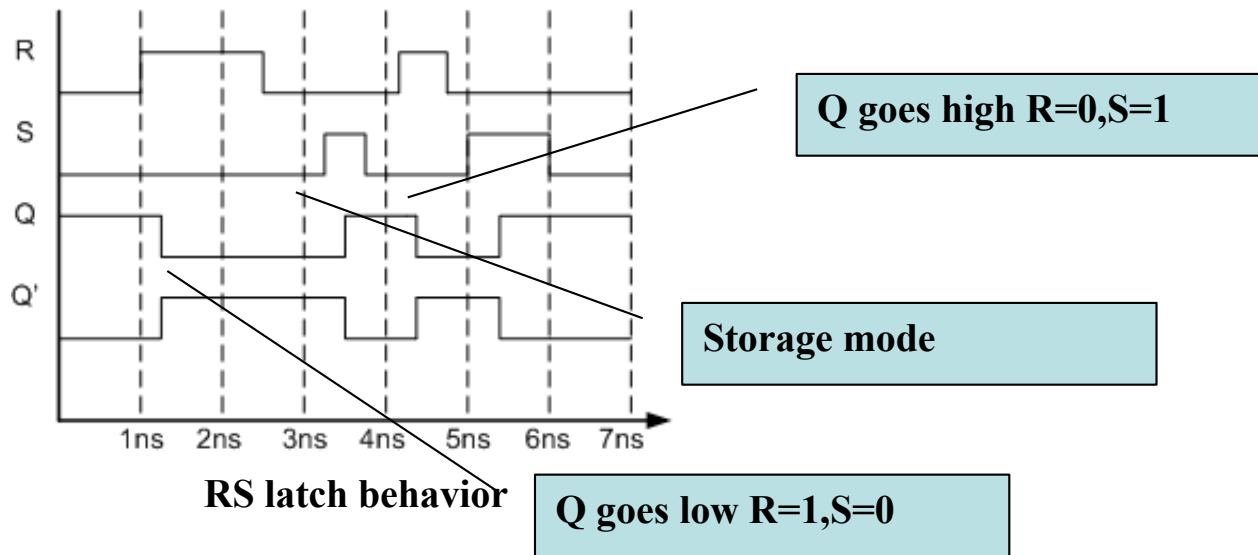

Signaling Behavior

 

D latch behavior


Q goes C=1, D=1

Q tracked D when C=1


Q went low C=1,D=0

Q stays low b/c C=0


Signaling Behavior

 


Signaling Behavior

 

RS latch behavior

 

D latch behavior

 



D flip-flop (falling edge triggered)

Example circuits and clocking

- Suppose we want to:
 - 1-bit value A stored in a D flip-flop
 - 1-bit value B stored in a D flip-flop
 - 1-bit value C stored in a D flip-flop
 - Do 1-bit addition of A and B, producing C


- $C = A + B$
 - What is the circuit?
 - Need three D flip-flops
 - Need one 1 bit adder

Example circuits and clocking

  

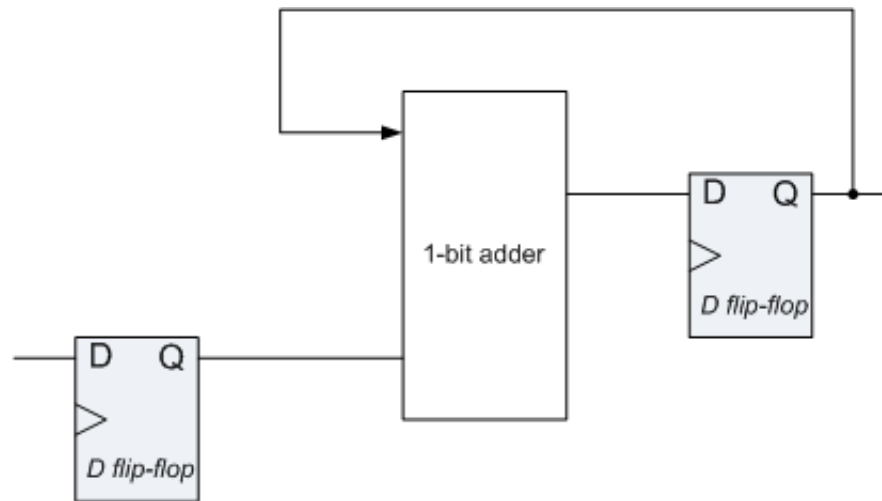Example circuits and clocking

- Is there any difference in the delay with this one?




- In fact, sequential logic often looks like this....

Example circuits and clocking

- Now, suppose we want to build a 4-bit counter?
 - Counter increments by 1 for a clock pulse (falling edge event)
 - 4 1-bit adders
 - 4 1-bit D flip-flops
- What's the circuit?
- How often to “pulse” the clock (increment counter)?

Example circuits and clocking

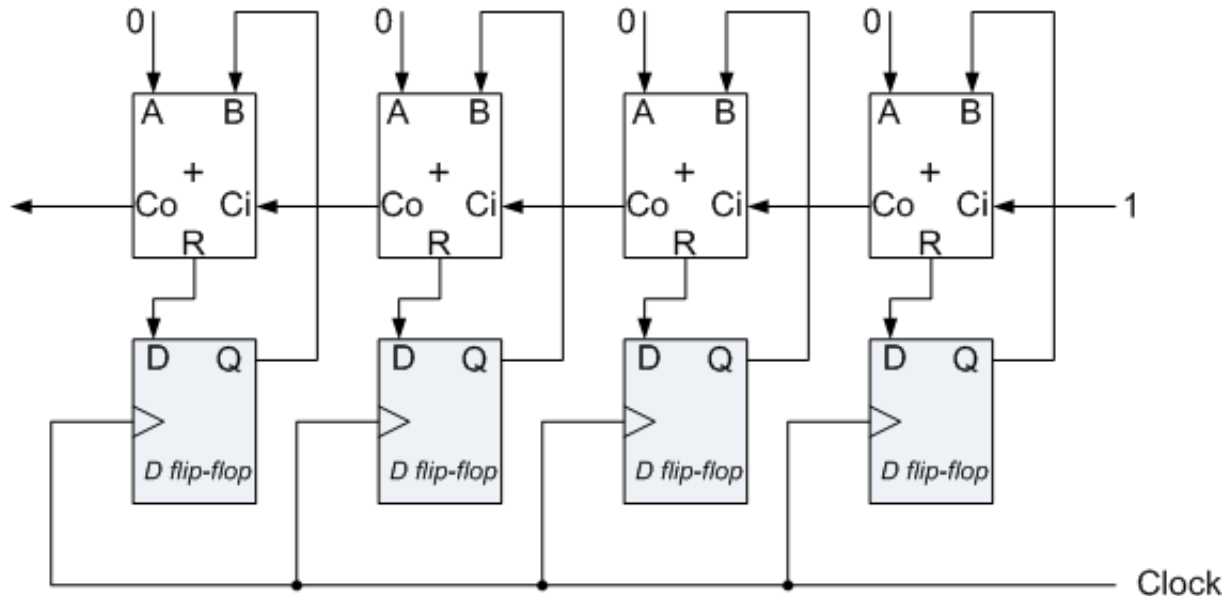

Recall: The flip-flops are edge triggered -- assuming falling edge (negative)

How often can an edge event happen?

No more frequent than the maximum propagation delay


Let's compute the delay -- assume 2ns for latch to stabilize and 4ns for adder

Example circuits and clocking

- Values of output bits *must all be stable*
 - I.e., can't pulse the clock (increment) until all four bits are computed
- Adder circuit is ripple-carry: Must wait for carries
 - 4ns per adder
 - 4-bit adder
 - thus, $4 * 4\text{ns} = 16\text{ns}$ for the adder
- Flip-flops
 - Must wait for 1st latch of last bit to stabilize (others done in parallel)
 - Must wait for 2nd latch of all bits to stabilize (all done in parallel)
 - thus, $2\text{ns} + 2\text{ns} = 4\text{ns}$
- Overall delay = $16\text{ns} + 4\text{ns} = 20\text{ns}$. Clock pulse is 20ns.

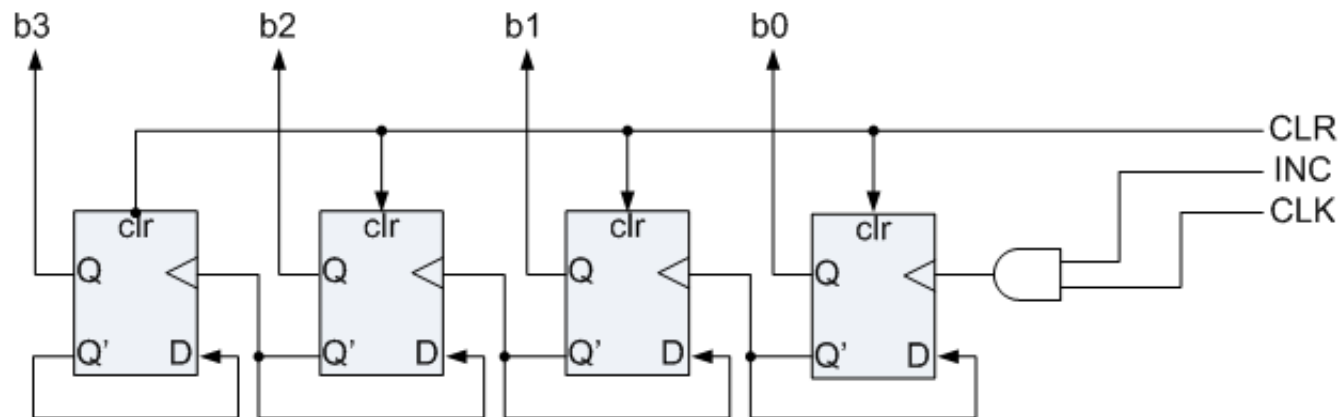Example circuits and clocking

Can we build a counter with just flip-flops?



What's the propagation delay?