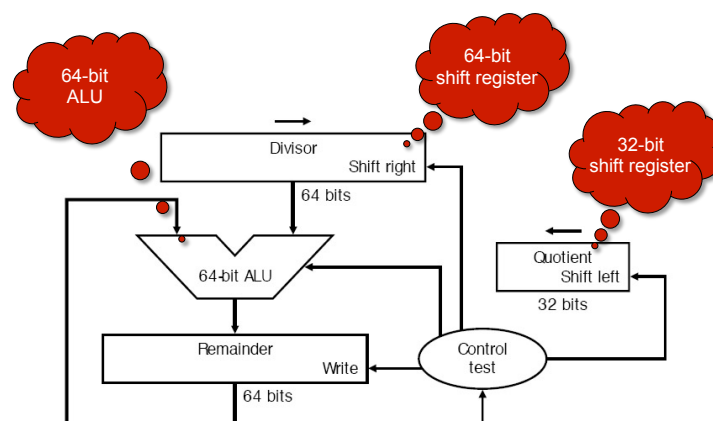



Binary division

- $\text{quotient} = \text{dividend} / \text{divisor}$, with a remainder
- $\text{dividend} = \text{divisor} \times \text{quotient} + \text{remainder}$
- Given dividend and divisor, we want to obtain quotient (Q) and remainder (R)
- We will start from our paper & pencil method

Hardware design 1



Hardware design 2

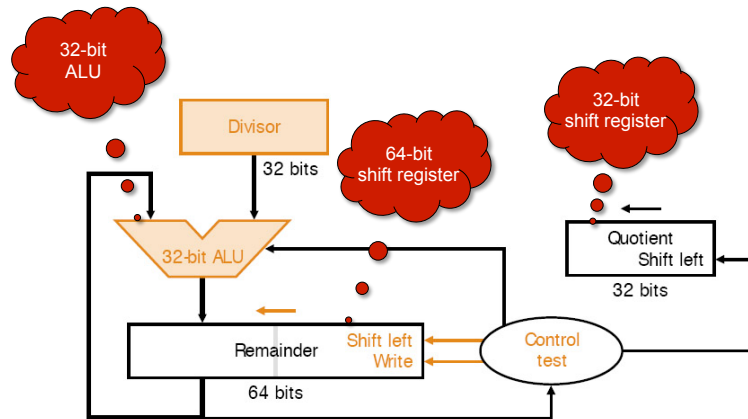


CS/CoE0447: Computer Organization and Assembly Language

University of Pittsburgh

4

Hardware design 3

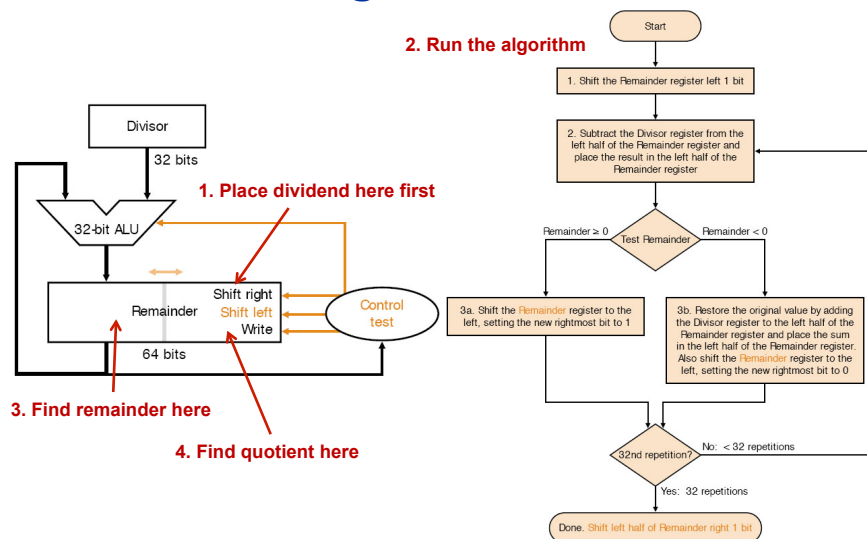

CS/CoE0447: Computer Organization and Assembly Language

University of Pittsburgh

5

Example

- Let's do 0111/0010 (7/2) – unsigned

Iteration	Divisor	Hardware design 3	
		Step	Remainder
0	0010	initial values	0000 0111
		shift remainder left by 1	0000 1110
1	0010	remainder = remainder – divisor	1110 1110
		(remainder<0) ⇒ +divisor; shift left; r0=0	0001 1100
2	0010	remainder = remainder – divisor	1111 1100
		(remainder<0) ⇒ +divisor; shift left; r0=0	0011 1000
3	0010	remainder = remainder – divisor	0001 1000
		(remainder>0) ⇒ shift left; r0=1	0011 0001
4	0010	remainder = remainder – divisor	0001 0001
		(remainder>0) ⇒ shift left; r0=1	0010 0011
done	0010	shift "left half of remainder" right by 1	0001 0011

Restoring division

- The three hardware designs we saw are based on the notion of “restoring division”
 - At first, attempt to subtract divisor from dividend
 - If the result of subtraction is negative – it rolls back by adding divisor
 - This step is called “restoring”
- It's a “trial-and-error” approach; can we do better?

Non-restoring division

- Let's revisit the restoring division designs
 - Given remainder R ($R < 0$) after subtraction
 - By adding divisor D back, we have $(R+D)$
 - After shifting the result, we have $2 \times (R+D) = 2 \times R + 2 \times D$
 - If we subtract the divisor in the next step, we have $2 \times R + 2 \times D - D = 2 \times R + D$
- This is equivalent to
 - Left-shifting R by 1 bit and then adding D !
- There's a "special case" when you finish with a negative
 - The negative value must be restored (add D back to R)

Example, non-restoring division

- Let's again do $0111/0010$ ($7/2$) – unsigned

Iteration	Divisor	Hardware design 3, non-restoring	
		Step	Remainder
0	0010	initial values	0000 0111
		shift remainder left by 1	0000 1110
1	0010	remainder = remainder – divisor	1110 1110
		(remainder < 0) \Rightarrow shift left; $r_0=0$	1101 1100
2	0010	remainder = remainder + divisor	1111 1100
		(remainder < 0) \Rightarrow shift left; $r_0=0$	1111 1000
3	0010	remainder = remainder + divisor	0001 1000
		(remainder > 0) \Rightarrow shift left; $r_0=1$	0011 0001
4	0010	remainder = remainder – divisor	0001 0001
		(remainder > 0) \Rightarrow shift left; $r_0=1$	0010 0011
done	0010	shift "left half of remainder" right by 1	0001 0011