 


Single vs. Multi-cycle Implementation

- Single cycle design is simple
- But it's inefficient
- Why?
 - All instructions have same clock cycle length - they all take the same amount of time regardless of what they actually do
- Clock cycle determined by longest path
 - Load: uses IM, RF, ALU, DM, RF in sequence
- But others may be shorter
 - R-type (arithmetic): use IM, RF, ALU, RF


73

Single Cycle: Load Word



74

Single Cycle: Load Word

 


75

Single vs. Multi-cycle Implementation

- Multicycle: Instructions take **several faster cycles**
- For this simple version, the multi-cycle implementation could be as much as **1.27 times faster** (for a typical instruction mix)
- Suppose we had floating point operations
 - Floating point has very high latency
 - E.g., floating-point multiply may be 16 ns vs integer add may be 2 ns
 - So, **clock cycle constrained by 16 ns of FP**
- Suppose a program doesn't do ANY floating point?
 - Performance penalty is too big to tolerate

76

Multi-cycle Implementation

 

- Single memory unit (I and D), single ALU
- Several temporary registers (IR, MDR, A, B, ALUOut)
- Temporaries hold output value of element so the output value can be used on subsequent cycle
- Values needed by subsequent instruction stored in programmer visible state (memory, RF)

77

A single ALU


- Single ALU must accommodate all inputs that used to go to three different ALUs in the single cycle implementation

1. Multiplexor on first input to ALU to select A register (from RF) or the PC
2. Multiplexor on second input to ALU to select from the constant 4 (PC increment), sign-extended value, shifted offset field, and RF input

- Trade-off: Additional multiplexors (and time) but only a single ALU since it can be shared across cycles

78

Multi-cycle Datapath with Control

 

- Datapath with additional muxes, temporary registers, and new control signals
- Most temporaries (except IR) are updated on every cycle, so no write control is required (always write)

79

Multi-cycle Steps - Instruction Fetch

- Instruction fetch


```
IR = Memory[PC] ;
PC = PC + 4;
```
- Operation
 - Send PC to memory as the address
 - Read instruction from memory
 - Write instruction into IR for use on next cycle
 - Increment PC by 4
 - Uses ALU in this first cycle
 - Set control signals to send PC and constant 4 to ALU

80

Multi-cycle Steps - Instruction Decode

- Don't yet know what instruction is
 - Decode the instruction concurrently with RF read
 - Optimistically read registers
 - Optimistically compute branch target
 - We'll select the right answer on next cycle
- Decode and Register File Read

```
A = Reg[IR[25-21]];
B = Reg[IR[20-16]];
ALUOut = PC + (sign-extend(IR[15-0]) << 2);
```

81

Multi-cycle Steps - Execution

- Operation varies based on instruction decode
- Memory reference:

```
ALUOut = A + sign-extend(IR[15-0]);
```
- Arithmetic-logical instruction:

```
ALUOut = A op B;
```
- Branch:

```
if (A == B) PC = ALUOut;
```
- Jump:

```
PC = PC[31-28] || (IR[25-0] << 2)
```

82

Multi-cycle Steps - Memory / Completion

- Load/store accesses memory or arithmetic writes result to the register file

- Memory reference:

`MDR = Memory[ALUOut]; (load)`

or

`Memory[ALUOut] = B; (store)`

- Arithmetic-logical instruction:

`Reg[IR[15-11]] = ALUOut;`

83

Multi-cycle Steps - Read completion

- Finish a memory read by writing read value into the register file

- Load operation:

`Reg[IR[20-16]] = MDR;`

84

Multi-cycle Steps

- Instructions always do the first two steps
- Branch can finish in the third step
- Arithmetic-logical can finish in the fourth step
- Stores can finish in the fourth step
- Loads finish in the fifth step

<u>Instruction</u>	<u>Number of cycles</u>
Branch / Jump	3
Arithmetic-logical	4
Stores	4
Loads	5

85

Multi-cycle vs. Single cycle?

- Why does it help?
- Let's consider a simple example.... in class example

86

Multi-cycle Instruction Execution

Branch

```
Cycle0:    IR=Memory[PC];
            PC=PC+4;
Cycle1:    ALUout=PC+(sign-extend(IR[15-0])<<2);
Cycle2:    if A=B PC=ALUout;
```

Arithmetic

```
Cycle0:    IR=Memory[PC];
            PC=PC+4;
Cycle1:    A=Reg[IR[25-21]]; B=Reg[IR[20-16]];
Cycle2:    ALUout = A op B;
Cycle3:    Reg[IR[15-11]]=ALUout;
```

88


Multi-cycle Instruction Execution

Load

```
Cycle0:    IR=Memory[PC];
            PC=PC+4;
Cycle1:    A=Reg[IR[25-21]];
Cycle2:    ALUout = A + sign-extend(IR[15-0]);
Cycle3:    MDR=Memory[ALUout];
Cycle4:    Reg[IR[20-16]]=MDR;
```

89

Multi-cycle Datapath with Control

 


90

Multi-cycle Control

Finite State Machine

 each cycle: advance one state
 in a state: set datapath control
 make decision based on opcode
 control is different after Decode



91

Multi-cycle Control

- How are the control signals set in each state?
- What are the transitions between states? (i.e., what state is next?)
- Control signals
 - IorD, MemRead, MemWrite, IRWrite, RegDst
 - MemtoReg, RegWrite, ALUSrcA
 - ALUSrcB, ALUOp
 - PCWrite
- Transitions from *Decode* based on Opcode
- Transitions from *Eff. Addr.* happen on load/store

93

Multi-cycle Control

- What are the control signals in each state for instrs:
 - Arithmetic
 - Load
 - Store
 - Branch
 - Jump

94

Control for each instruction type?

	STATE (CYCLE NUMBER, ADVANCE EACH CYCLE)				
CONTROL	FETCH(1)	DECODE(2)	STATE 3	STATE 4	STATE 5
lOrD					
MemRead					
MemWrite					
IRWrite					
RegDst					
MemToReg					
RegWrite					
ALUSrcA					
ALUSrcB					
ALUOp					
PCWrite					

95

Control for addition (arithmetic)

	STATE (CYCLE NUMBER, ADVANCE EACH CYCLE)				
CONTROL	FETCH(1)	DECODE(2)	EXE ALU(3)	WB ALU(4)	STATE 5
lOrD	0	X	X	X	
MemRead	1	0	0	0	
MemWrite	0	0	0	0	
IRWrite	1	0	0	0	
RegDst	X	X	X	1	
MemToReg	X	X	X	0	
RegWrite	0	0	0	1	
ALUSrcA	0	0	1	X	
ALUSrcB	01	11	00	X	
ALUOp	00	00	10	X	
PCWrite	1	0	0	0	

97

Control for addition (load)

	STATE(CYCLE NUMBER, ADVANCE EACH CYCLE)				
CONTROL	FETCH(1)	DECODE(2)	EFF AD(3)	MEM RD(4)	WB MEM(5)
lOrD	0	X	X	1	X
MemRead	1	0	0	1	0
MemWrite	0	0	0	0	0
IRWrite	1	0	0	0	0
RegDst	X	X	X	X	0
MemToReg	X	X	X	X	1
RegWrite	0	0	0	0	1
ALUSrcA	0	0	1	X	X
ALUSrcB	01	11	10	X	X
ALUOp	00	00	10	X	X
PCWrite	1	0	0	0	0


98

Finite state machine (FSM)

Need a way to specify control per cycle

FSM: Tracks “step of execution” to generate control signals

 
Implementation: Generally, “**hardwired**” or “microcode”



99


Traffic light control example

- Two states
 - NSgreen: green light on North-South road
 - EWgreen: green light on East-West road
- Sensors (inputs) in each lane to detect car
 - NScar: a car in either the north or south bound lanes
 - EWcar: a car in either the east or west bound lanes
- Control signals (outputs) to each light
 - NSlite: 0 is red, 1 is green
 - EWlite: 0 is red, 1 is green
- Current state goes for 30 seconds, then
 - Switch to the other state if there is a car waiting
 - Current state goes for another 30 seconds if not
- We use 1/30 Hz clock (Hz is clock cycles per second)
 - I.e., determine a new state (possibly current one) every thirty seconds

 

100

Traffic light control example

 

101


Traffic light control example

Current state	Inputs		Next state
	NScar	EWcar	
NSgreen	0	0	NSgreen
NSgreen	0	1	EWgreen
NSgreen	1	0	NSgreen
NSgreen	1	1	EWgreen
EWgreen	0	0	EWgreen
EWgreen	0	1	EWgreen
EWgreen	1	0	NSgreen
EWgreen	1	1	NSgreen

Current state	Outputs	
	NSlite	EWlite
NSgreen	1	0
EWgreen	0	1

102

Traffic light control example

 

103

Traffic light control example

- Let's assign "0" to NSlite and "1" to EWlite initially
- $\text{NextState} = \text{CurrentState}' \cdot \text{EWcar} + \text{CurrentState} \cdot \text{NScar}'$
- $\text{NSlite} = \text{CurrentState}'$
- $\text{EWlite} = \text{CurrentState}$
- see carfsm.circ on 447 web site