




Designing the Processor

Datapath & Control (review of Sec. 4.1 – 4.4)




Review of Single cycle implementation

 
- **Simplified to contain only:**
 - memory-reference instructions: `lw`, `sw`
 - arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `slt`
 - control flow instructions: `beq`
- **Generic Implementation:**
 - The program counter (PC) supplies instruction address
 - get the instruction from the “instruction memory”
 - the op-code determines exactly what to do.



R-type

 


I-type (`lw`, `sw`, `beq`)

 

J-type


MIPS instruction format and architecture

Fetching instruction and incrementing PC

 

3

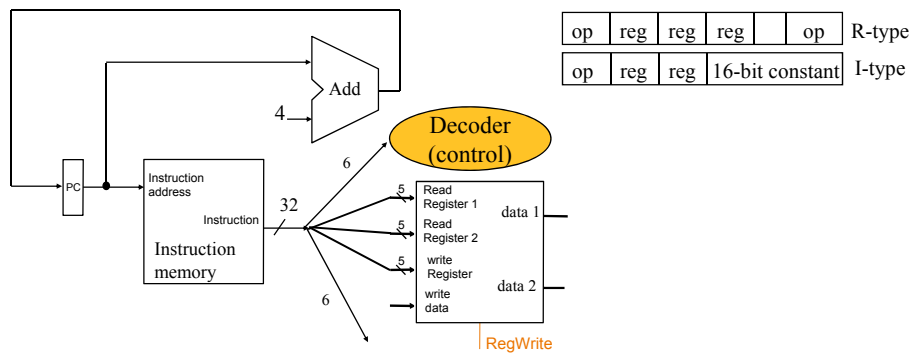The first two steps of executing instructions




- 1) Fetch and increment PC
- 2) Read registers

The control unit should decode the op-code to determine what to do next
- depends on instruction type

4

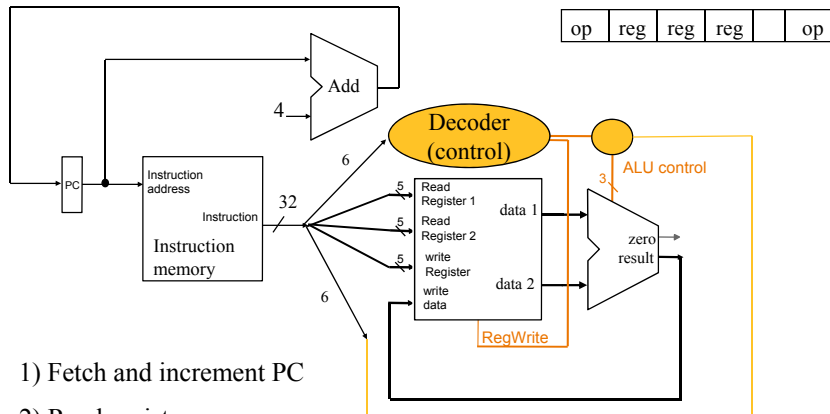Executing *R-type* instructions (in one cycle)




- 1) Fetch and increment PC
- 2) Read registers
- 3) Execute operation
- 4) Store result

The control unit issues:

- the corresponding ALU control
- RegWrite signal

5


Executing *sw* instructions

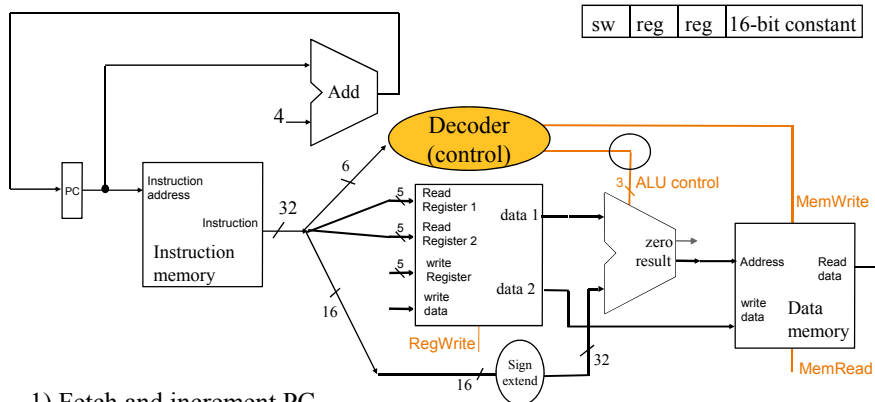


- 1) Fetch and increment PC
- 2) Read registers
- 3) Calculate memory address (issue ALU control signals – add)
- 4) Write data to memory (issue MemWrite signal)

6

Data path conflicts

 

Path for R-type

 

Path for sw


- 1) The second input to the ALU comes from two different places
- 2) The data2 output goes to two different places
- 3) The output of the ALU goes to two different places

7


Reconciling data paths



 - 1) No problems in fanning out one signal to two points




 - 2) Cannot connect two signals to one point (should use multiplexers)



8


Resolving data path conflicts

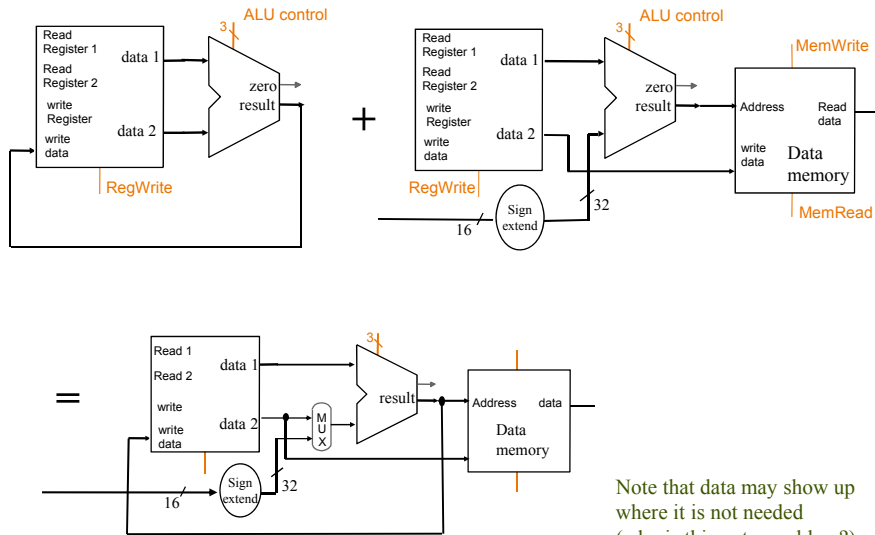

Note that data may show up where it is not needed (why is this not a problem?)

9

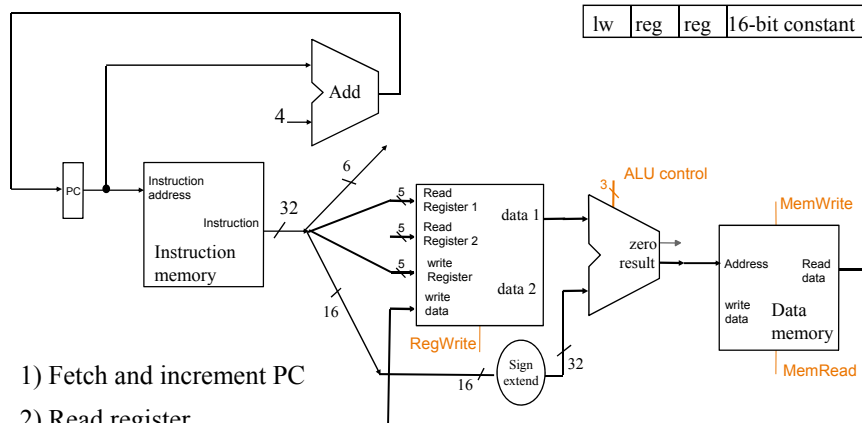
Executing *lw* instructions (in one cycle)



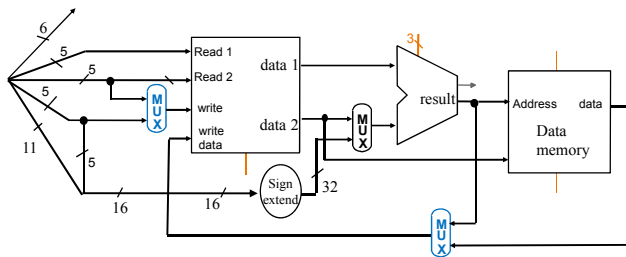- 1) Fetch and increment PC
- 2) Read register
- 3) Calculate memory address (issue ALU control signals – add)
- 4) Read data from memory (issue MemRead signal)
- 5) Store data in register (issue Regwrite signal)


10

Reconciling *R-type*, *sw* and *lw* data paths



11

Executing *beq* instructions

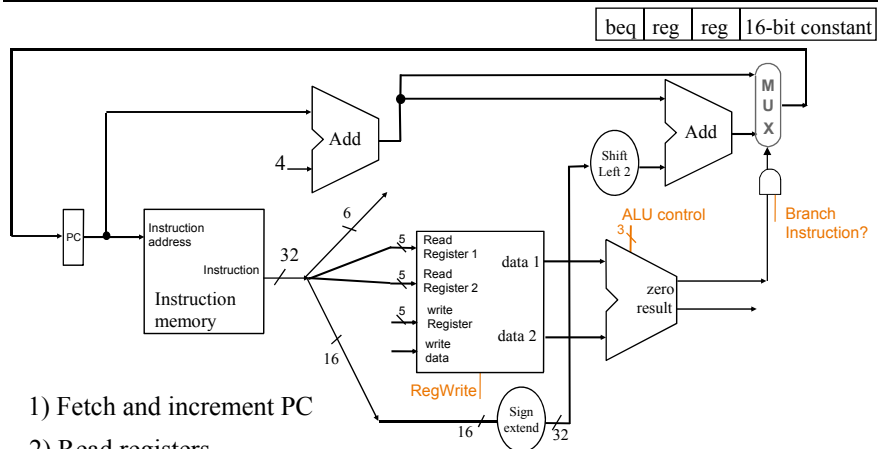


- 1) Fetch and increment PC
- 2) Read registers
- 3) Calculate branch condition (issue ALU control signals – subtract)
- 4) Calculate target address
- 5) Select next PC depending on the result in 3

12


Control



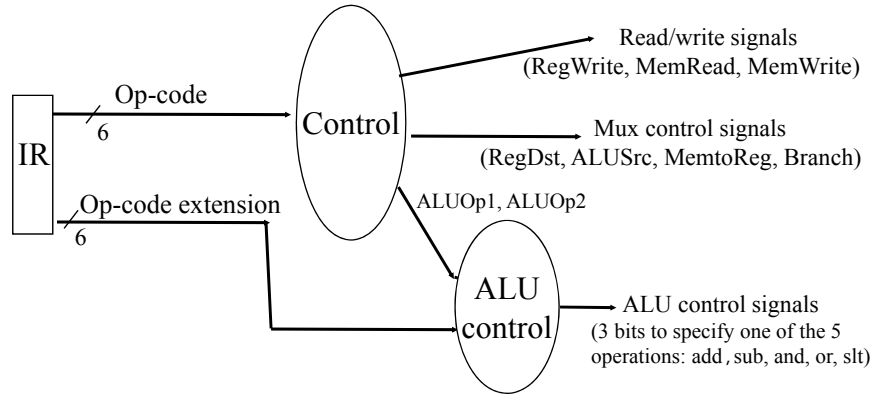- Using the op-code from the instruction, the control issues signals to:
 - select the operations to perform (ALU, read/write to registers and memory)
 - control the flow of data (multiplexor inputs).



13

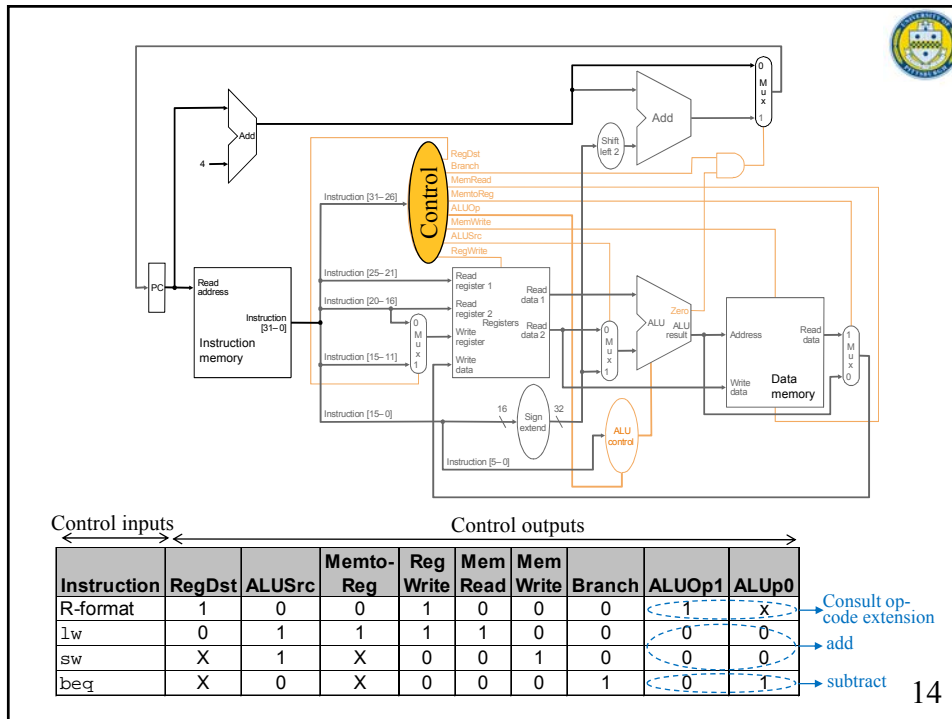


14

The one cycle CPU implementation



 - Use combinational logic to generate control signals
- Should wait for everything to settle down, and the right thing to be done
- Cycle time determined by length of the longest path




15

Single Cycle Implementation



Assume negligible delays for all components except:
memory (0.2ns), ALU and adders (0.2ns), register file access (0.1ns)

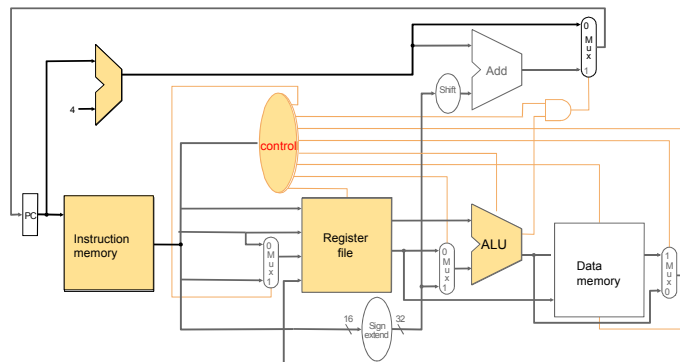- **Question:** calculate the time to execute an *R-type* instruction
- **Answer:** 0.2ns to read instruction + 0.1ns to read registers + 0.2ns for ALU operation + 0.1 n.sec to write into register = 0.6ns




16

Single Cycle Implementation (lw)



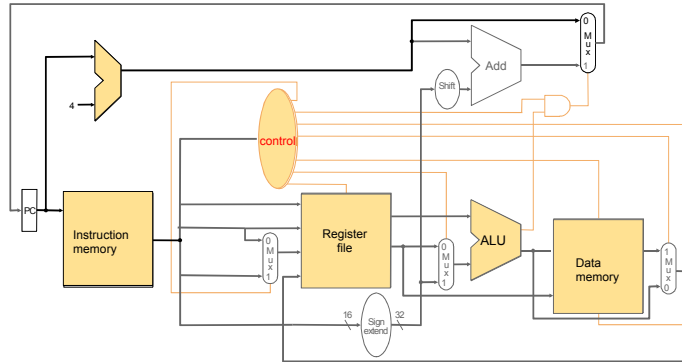- Similarly, the following is needed to execute the *lw* instructions:
- 0.2ns to read instruction + 0.1ns to read registers + 0.2ns for ALU operation + 0.2ns to read from data memory + 0.1 n.sec to write into register = 0.8ns .



- Can calculate that *sw* takes 0.7ns , and *branch* take 0.5ns
- **Hence**, the cycle time of the machine should be large enough to execute every instruction. That is 0.8ns .